



State Machine Outputs and Logic Glitches

Announcements

- Homework #10 due Today
- Homework #11 due in one week
- Exam #3 Monday
 - Study Jam
 - Study Topics will be posted
- Read Chapter 11 Sections 1-4



Exam #3 Study Jam

Sunday November 17, 2019

12:00 - 4:00 pm

GOL 1360

Bring questions

State Machine VHDL in ECTET


- We follow a 3 (+) process model for state machines
 - Synchronizing process
 - `Current_state <= next_state`
 - Combinational process
 - Sets up the `next_state` signal
 - `Next_state` should be the only output from this process
 - Output process(es)
 - Each state machine output should have its own process

State Machine VHDL in ECTET

- Any counters or timers that are needed should also be in their own process

Synchronizing FSM outputs

- FSM with unsynchronized outputs

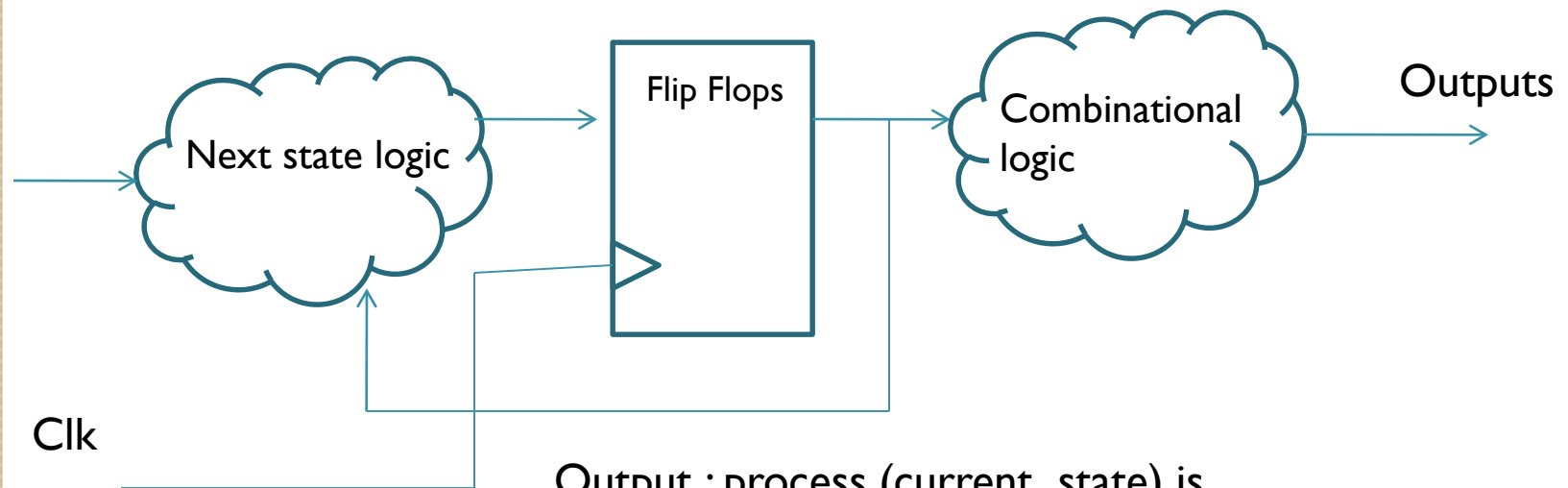

Problem?

*Combinational logic on
Output prone to glitches*

Output : process (current_state) is
begin

if current_state = A or current_state = B then
outputAB <= '1';

else


outputAB <= '0';

end if;

end process;

Synchronizing FSM outputs

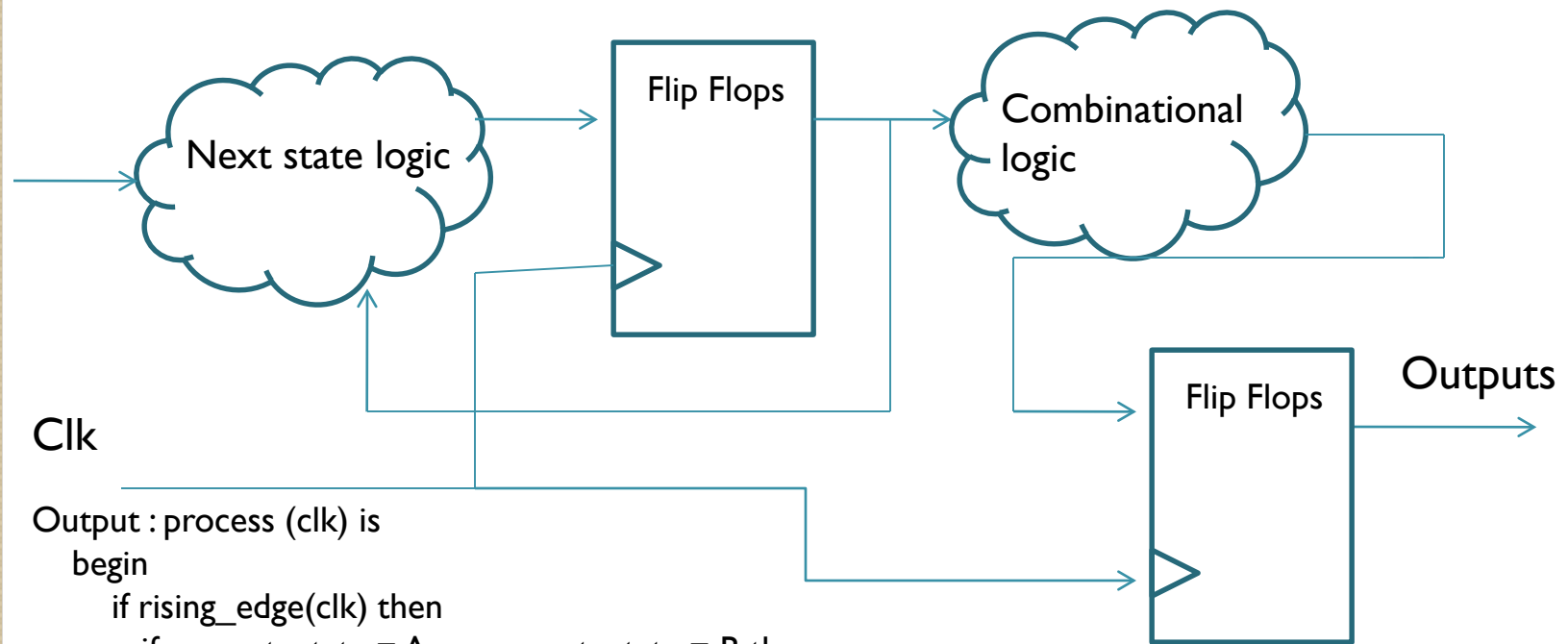- This would solve the potential glitch problem




```
Output : process (clk) is
begin
  if rising_edge(clk) then
    if current_state = A or current_state = B then
      outputAB <= '1';
    else
      outputAB <= '0';
    end if;
  end if;
end if;
end process;
```

Problem?

Outputs are delayed by 1 clock cycle

Synchronizing FSM outputs

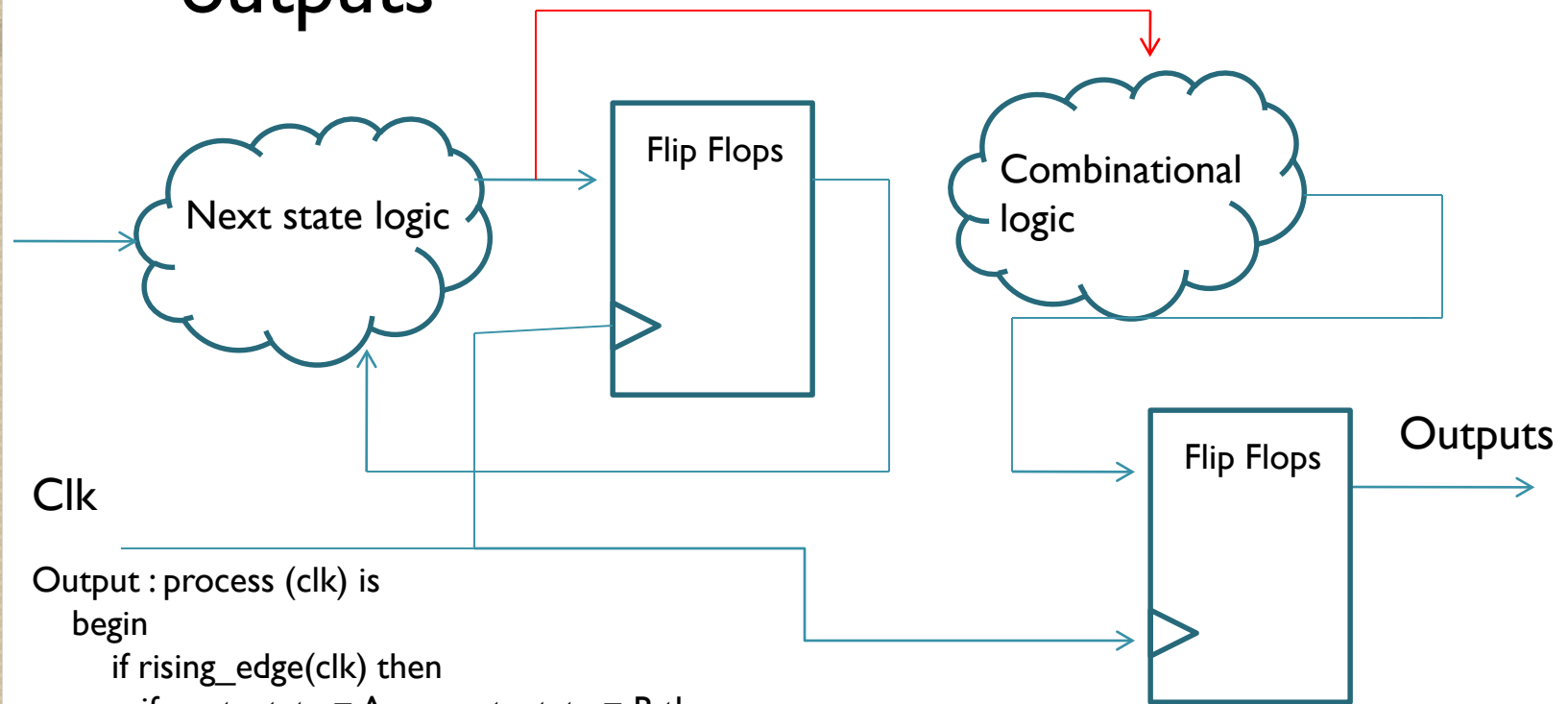- Solve the problem without delaying outputs




```
Output : process (clk) is
begin
  if rising_edge(clk) then
    if next_state = A or next_state = B then
      outputAB <= '1';
    else
      outputAB <= '0';
    end if;
  end if;
end process;
```


FSM VHDL example

Always Start With State Transition Diagram

State	Left	Right
Forward	1	1
Back	0	0
TurnR	1	0
TurnL	0	1

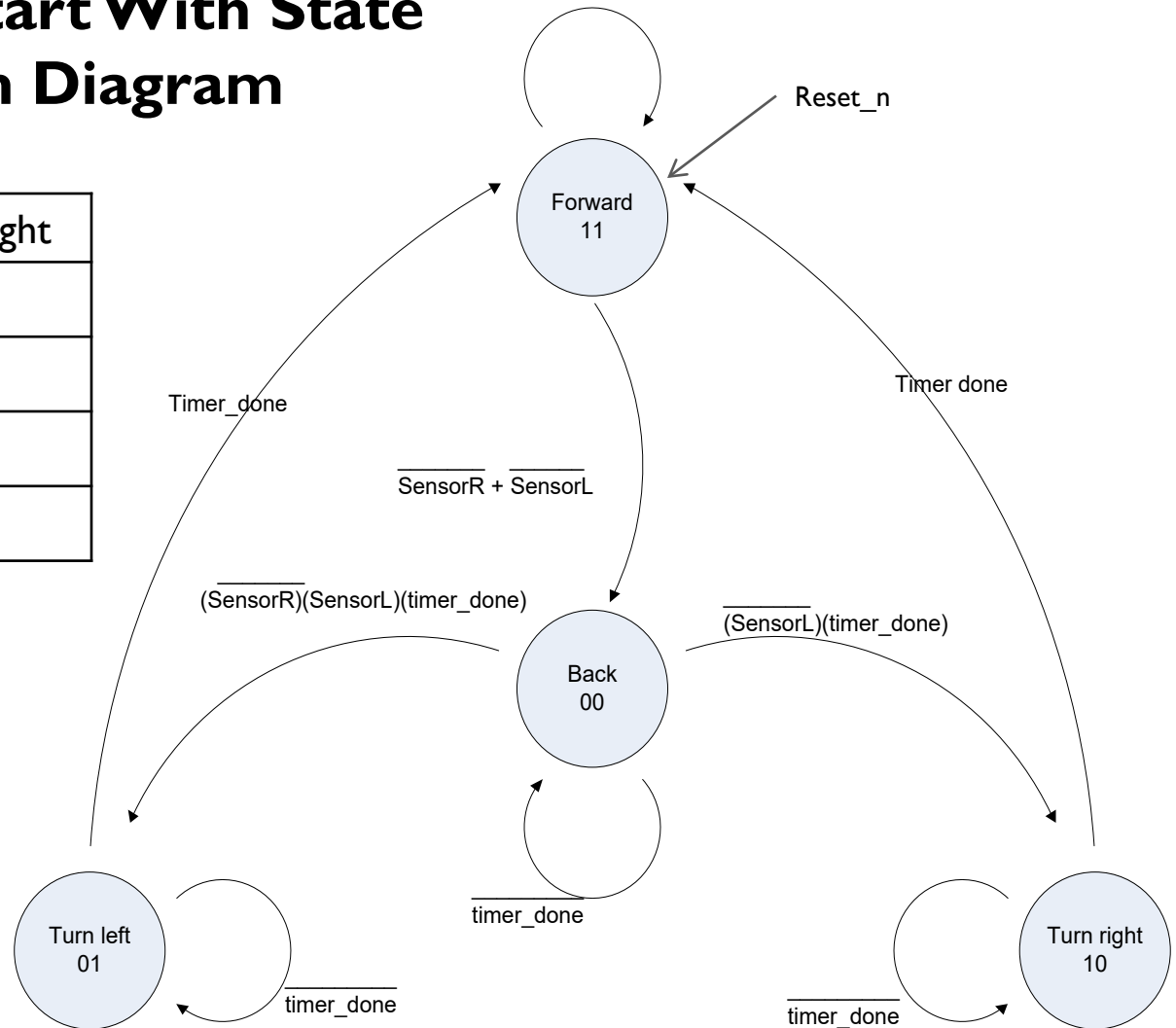

FSM VHDL example

- Enumerated State Type
- Synchronizing process

FSM VHDL example

- Combinatorial process (next state logic)

FSM VHDL example


- Outputs



Timing Diagrams and Logic Glitches

Simple Glitch

 - A simple glitch can occur because not all signals change at the same time due to varying path lengths




Definitions

- Steady-State Behavior
 - Assumes inputs have been stable for a long time
- Transient Behavior
 - Takes into account circuit delays
- Hazards
 - An unintended change in output value
 - The digital circuit is **logically correct** but the output is incorrect

Static hazards


- Static-1 hazard

 - Output was expected to stay high, but glitches low momentarily



- Static-0 hazard

 - Output was expected to stay low but glitches high momentarily




- Causes

- When a single input has two different paths to the output and the paths are different lengths
- Each path has a different prop delay

Static Hazard Example

- Determine F assuming no prop delay

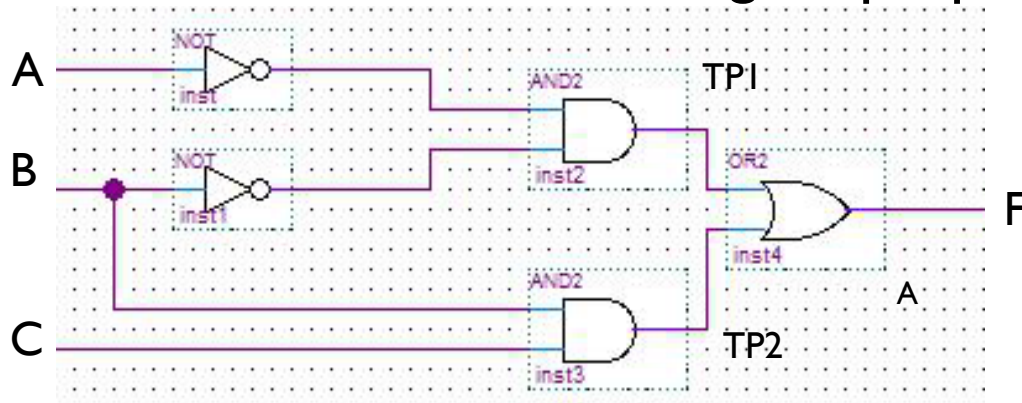


B

C

TP1



TP2

F

 

Static Hazard example

- Now add prop delays (assume 1 unit)

 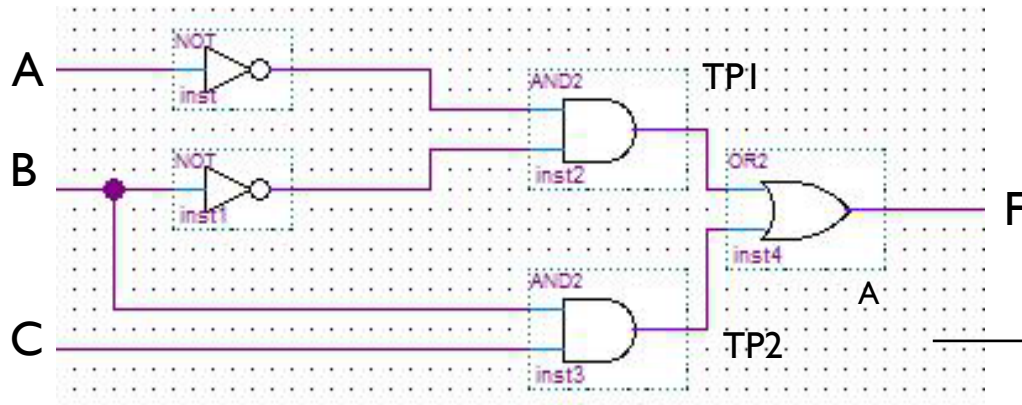

Why do hazards Matter?

- Often the output of one circuit is the input of another
 - Input could be read at a precise moment in time
 - Input could drive clocked logic
 - Output could be controlling logic such as a traffic light

