

Kirchhoff's Law

MATH 211

- Suppose that in a simple circuit the resistance is $12\ \Omega$ and the inductance is $4\ \text{H}$. If the battery gives a constant voltage of $60\ \text{V}$ and the switch is closed at $t = 0$ so the initial current is 0 , find the current as a function of time.

$$L \frac{di}{dt} + Ri = E(t)$$

$$4 \frac{di}{dt} + 12i = 60$$

$$\frac{di}{dt} + 3i = 15$$

$$e^{3t} \left[\frac{di}{dt} + 3i \right] = 15e^{3t}$$

$$\frac{d}{dt} [ie^{3t}] = 15e^{3t}$$

$$d [ie^{3t}] = 15e^{3t} dt$$

$$\int d [ie^{3t}] = 15 \int e^{3t} dt$$

$$ie^{3t} = \frac{15}{3} e^{3t} + K$$

$$ie^{3t} = 5e^{3t} + K$$

$$i = 5 + Ke^{-3t}$$

$$0 = 5 + Ke^0$$

$$-5 = K$$

$$i = 5 - 5e^{-3t}$$

$$e^{\int P(t) dt}$$

$$= e^{\int 3 dt}$$

$$= e^{3t}$$

2. Suppose that in a simple circuit the resistance is 12Ω and the inductance is 4 H . If a battery gives a voltage of $E(t) = 60 \sin(30t) \text{ V}$ and the switch is closed at $t = 0$ so the initial current is 0 , find the current as a function of time.

$$L \frac{di}{dt} + Ri = E(t)$$

$$4 \frac{di}{dt} + 12i = 60 \sin(30t)$$

$$\frac{di}{dt} + 3i = 15 \sin(30t)$$

$$e^{3t} \left[\frac{di}{dt} + 3i \right] = 15e^{3t} \sin(30t)$$

$$\frac{d}{dt} [ie^{3t}] = 15e^{3t} \sin(30t)$$

$$d [ie^{3t}] = 15e^{3t} \sin(30t) dt$$

$$\int d [ie^{3t}] = 15 \int e^{3t} \sin(30t) dt$$

$$ie^{3t} = -\frac{10}{303} e^{3t} \cos(30t) + \frac{1}{303} e^{3t} \sin(30t) + K$$

$$i = -\frac{10}{303} \cos(30t) + \frac{1}{303} \sin(30t) + Ke^{-3t}$$

$$0 = -\frac{10}{303}(1) + \frac{1}{303}(0) + Ke^0$$

$$K = \frac{10}{303}$$

$$i = -\frac{10}{303} \cos(30t) + \frac{1}{303} \sin(30t) + \frac{10}{303} e^{-3t}$$

$$\star \int e^{3t} \sin(30t) dt$$

$$\begin{array}{ll} u = e^{3t} & dv = \sin(30t) dt \\ du = 3e^{3t} dt & v = -\frac{1}{30} \cos(30t) \end{array}$$

$$\int e^{3t} \sin(30t) dt = -\frac{1}{30} e^{3t} \cos(30t) + \frac{1}{10} \int e^{3t} \cos(30t) dt$$

$$\begin{array}{ll} u = e^{3t} & dv = \cos(30t) dt \\ du = 3e^{3t} dt & v = \frac{1}{30} \sin(30t) \end{array}$$

$$\int e^{3t} \sin(30t) dt = -\frac{1}{30} e^{3t} \cos(30t) + \frac{1}{10} \left[\frac{1}{30} e^{3t} \sin(30t) - \frac{1}{10} \int e^{3t} \sin(30t) dt \right]$$

$$\int e^{3t} \sin(30t) dt = -\frac{1}{30} e^{3t} \cos(30t) + \frac{1}{300} e^{3t} \sin(30t) - \frac{1}{100} \int e^{3t} \sin(30t) dt$$

$$\frac{101}{100} \int e^{3t} \sin(30t) dt = -\frac{1}{30} e^{3t} \cos(30t) + \frac{1}{300} e^{3t} \sin(30t) + K$$

$$\int e^{3t} \sin(30t) dt = \frac{100}{101} \left[-\frac{1}{30} e^{3t} \cos(30t) + \frac{1}{300} e^{3t} \sin(30t) + K \right]$$

$$\int e^{3t} \sin(30t) dt = -\frac{10}{303} e^{3t} \cos(30t) + \frac{1}{303} e^{3t} \sin(30t) + K$$

$$\begin{aligned} & e^{\int P(t) dt} \\ &= e^{\int 3 dt} \\ &= e^{3t} \end{aligned}$$

3. In a simple circuit, a battery supplies a constant voltage of 40 V, the inductance is 2 H and the resistance is 10 Ω . If the initial current is 0, find the current as a function of time.

$$L \frac{di}{dt} + Ri = E(t)$$

$$2 \frac{di}{dt} + 10i = 40$$

$$\frac{di}{dt} + 5i = 20$$

$$e^{5t} \left[\frac{di}{dt} + 5i \right] = 20e^{5t}$$

$$\frac{d}{dt} [ie^{5t}] = 20e^{5t}$$

$$d [ie^{5t}] = 20e^{5t} dt$$

$$\int d [ie^{5t}] = 20 \int e^{5t} dt$$

$$ie^{5t} = \frac{20}{5} e^{5t} + K$$

$$i = 4 + Ke^{-5t}$$

$$0 = 4 + Ke^0$$

$$K = -4$$

$$i = 4 - 4e^{-5t}$$

$$e^{\int P(t) dt}$$

$$= e^{\int 5 dt}$$

$$= e^{5t}$$

4. A circuit contains an electromotive force, a capacitor with capacitance of C farads and a resistor with resistance R ohms. The voltage drop across the capacitor is Q/C where Q is the charge (in coulombs). Suppose the resistance is $5\ \Omega$, the capacitance is $0.05\ \text{F}$ and a battery gives a constant voltage of $60\ \text{V}$. If the initial charge in the circuit is 0 , find the charge and current as functions of time t .

$$R \frac{dQ}{dt} + \frac{Q}{C} = E(t)$$

$$5 \frac{dQ}{dt} + \frac{Q}{(1/20)} = 60$$

$$5 \frac{dQ}{dt} + 20Q = 60$$

$$\frac{dQ}{dt} + 4Q = 12$$

$$e^{4t} \left[\frac{dQ}{dt} + 4Q \right] = 12e^{4t}$$

$$\frac{d}{dt} [Qe^{4t}] = 12e^{4t}$$

$$d[Qe^{4t}] = 12e^{4t} dt$$

$$\int d[Qe^{4t}] = 12 \int e^{4t} dt$$

$$Qe^{4t} = \frac{12}{4}e^{4t} + K$$

$$Q = 3 + Ke^{-4t}$$

$$0 = 3 + Ke^0$$

$$K = -3$$

$$Q = 3 - 3e^{-4t}$$

$$i = \frac{dQ}{dt} = 0 - 3(-4e^{-4t}) = 12e^{-4t}$$