

Name: _____

Section: _____

R.I.T SCHOOL OF MATHEMATICAL SCIENCES

22 - Kirchhoff's Law

MATH 211

State the first order differential equation whose solution models the current over an RLC circuit as a function of time (Kirchhoff's Law).

$$L \frac{di}{dt} + Ri + \frac{q}{C} = E(t)$$

The current in a circuit is equal to the rate of change of the charge with respect to time. Write the relationship between current i and charge q .

$$\frac{dq}{dt} = i$$

$$\frac{d^2q}{dt^2} = \frac{di}{dt}$$

Write Kirchhoff's Law in the second order. What will the solution to this differential equation represent?

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = E(t)$$

$$Lq''(t) + Rq'(t) + \frac{q(t)}{C} = E(t)$$

The solution to this equation represents the charge as a function of time.

Find the current as a function of time for a circuit in which $L = 2 \text{ H}$, $R = 20 \Omega$, $C = 2000 \mu\text{F}$ and $E(t) = 2e^{-5t} \text{ V}$, if the initial charge is $\frac{1}{225} \text{ C}$ and the initial current is 0 A .

$$C = 2000 \mu\text{F} = 2000 \times 10^{-6} \text{ F} = \frac{1}{500} \text{ F}$$

$$Lq'' + Rq' + \frac{q}{C} = E(t)$$

$$2q'' + 20q' + \frac{q}{1/500} = 2e^{-5t}$$

$$2q'' + 20q' + 500q = 2e^{-5t}$$

$$q'' + 10q' + 250q = e^{-5t}$$

Complementary:

$$q'' + 10q' + 250q = 0$$

$$m^2 + 10m + 250 = 0$$

$$m = \frac{-10 \pm \sqrt{10^2 - 4(1)(250)}}{2(1)}$$

$$m = -5 \pm 15i$$

$$q_c = e^{-5t} [c_1 \sin(15t) + c_2 \cos(15t)]$$

Particular:

$$q_p = Ae^{-5t}$$

$$q'_p = -5Ae^{-5t}$$

$$q''_p = 25Ae^{-5t}$$

$$q''_p + 10q'_p + 250q_p = e^{-5t}$$

$$25Ae^{-5t} + 10(-5Ae^{-5t}) + 250Ae^{-5t} = e^{-5t}$$

$$225Ae^{-5t} = e^{-5t}$$

$$225A = 1$$

$$A = \frac{1}{225}$$

$$q_p = \frac{1}{225}e^{-5t}$$

$$q = q_c + q_p$$

$$q = e^{-5t} [c_1 \sin(15t) + c_2 \cos(15t)] + \frac{1}{225}e^{-5t}$$

$$q = e^{-5t} [c_1 \sin(15t) + c_2 \cos(15t)] + \frac{1}{225}e^{-5t}$$

$$\frac{1}{225} = (1) [c_1(0) + c_2(1)] + \frac{1}{225}(1)$$

$$\frac{1}{225} = c_2 + \frac{1}{225}$$

$$c_2 = 0$$

$$q = e^{-5t} [c_1 \sin(15t) + 0] + \frac{1}{225}e^{-5t}$$

$$q' = -5e^{-5t} c_1 \sin(15t) + 15e^{-5t} c_1 \cos(15t)$$

$$-\frac{1}{45}e^{-5t}$$

$$0 = -5c_1(0) + 15c_1(1) - \frac{1}{45}$$

$$15c_1 = \frac{1}{45}$$

$$c_1 = \frac{1}{675}$$

$$q = \frac{1}{675}e^{-5t} \sin(15t) + \frac{1}{225}e^{-5t}$$

$$i = -\frac{1}{135}e^{-5t} \sin(15t) + \frac{1}{45}e^{-5t} \cos(15t) - \frac{1}{45}e^{-5t}$$

Consider the RLC circuit with inductance 1 H, resistance 100 Ω and a capacitance of 400 μF with a voltage source of 30 V. The initial current is 2A and the initial charge is 0 C. Find the charge as a function of time.

$$C = 400 \mu\text{F} = 400 \times 10^{-6} \text{ F} = \frac{1}{2500} \text{ F}$$

$$Lq'' + Rq' + \frac{q}{C} = E(t)$$

$$q'' + 100q' + \frac{q}{1/2500} = 30$$

$$q'' + 100q' + 2500q = 30$$

Complementary:

$$q'' + 100q' + 2500q = 0$$

$$m^2 + 100m + 2500 = 0$$

$$(m + 50)^2 = 0$$

$$m_1 = m_2 = -50$$

$$q_c = c_1 e^{-50t} + c_2 t e^{-50t}$$

Particular:

$$q_p = A$$

$$q'_p = 0$$

$$q''_p = 0$$

$$q''_p + 100q'_p + 2500q_p = 30$$

$$0 + 0 + 2500A = 30$$

$$A = \frac{3}{250}$$

$$q_p = \frac{3}{250}$$

$$q = q_c + q_p$$

$$q = c_1 e^{-50t} + c_2 t e^{-50t} + \frac{3}{250}$$

$$q = c_1 e^{-50t} + c_2 t e^{-50t} + \frac{3}{250}$$

$$0 = c_1 e^0 + c_2(0)e^0 + \frac{3}{250}$$

$$0 = c_1 + \frac{3}{250}$$

$$c_1 = -\frac{3}{250}$$

$$q = -\frac{3}{250}e^{-50t} + c_2 t e^{-50t} + \frac{3}{250}$$

$$q' = \frac{3}{5}e^{-50t} - 50c_2 t e^{-50t} + c_2 e^{-50t}$$

$$2 = \frac{3}{5}e^0 - 50c_2(0)e^0 + c_2 e^0$$

$$2 = \frac{3}{5} + c_2$$

$$c_2 = \frac{7}{5}$$

$$q = -\frac{3}{250}e^{-50t} + \frac{7}{5}t e^{-50t} + \frac{3}{250}$$