



# Variables, VHDL Rules and Synthesis

# Final Exemption

- Students with an **A or an A-** in lecture AND an **A** in lab may be exempt from the DSD final.
  - Decisions will not be made until all graded items are submitted.
  - **This includes lab I I and quiz 7**

93.00 – 100.00	A
90.00 – 92.99	A-
87.00 – 89.99	B+
83.00 – 86.99	B
80.00 – 82.99	B-
77.00 – 79.99	C+
73.00 – 76.99	C
70.00 – 72.99	C-
60.00 – 69.99	D
00.00 – 59.99	F

\*If you take the final and your grade is higher than one of your previous exams, your final grade will replace your lowest exam grade.

# Variables

- Used to store intermediate values in a process or subprogram
  - can only be accessed from a single process or subprogram in which it is declared
- Declared like a signal
  - `VARIABLE count : std_logic_vector(3 downto 0);`
- Assignments made with `:=`
  - `Count := "0000";`

# Variables

- Declared in the process before the BEGIN statement
- Take the value assigned to them immediately
  - Similar to a traditional programming language
  - Remember signals don't get assigned until the end of the process
- Order matters because they are updated immediately

# Variable vs. Signal

- Signals represent wires or registers (when in a synchronous process)
- Variables store intermediate values and do not synthesize to hardware components
- They cannot be used interchangeably

# Variable Example

Here variable is used to store an intermediate value

```
entity generic_xor is
    generic(wide           : integer := 8);
    port(in_vect          : in std_logic_vector(wide-1 downto 0);
          y               : out std_logic);
end generic_xor;

architecture model of generic_xor is

    begin


        xorit: process (in_vect)
            variable tmp: std_logic;
            BEGIN
                tmp := '0';
                for i in wide-1 downto 0 LOOP
                    tmp := tmp XOR in_vect(i);
                end LOOP;
                y <= tmp ;
            END PROCESS;

        end model;
```
 
# Variable vs. Signal Example

```
xor_var: process (in_vect)
    variable tmp: std_logic;
BEGIN
    tmp := '0';
    for i in 7 downto 0 LOOP
        tmp := tmp XOR in_vect(i);
    end LOOP;
    y_var <= tmp ;
END PROCESS;
```

```
xor_sig: process (in_vect)
BEGIN
    for i in 7 downto 0 loop
        x_sig <= x_sig xor in_vect(i);
    end loop;
    y_sig <= x_sig ;
end process;
```




# Variable vs. Signal Example

```
entity regs is
  port(d, clk      : in std_logic;
        q          : out std_logic);
end regs;
```

```
architecture behave of regs is
  signal a,b : std_logic;
```
 
```
Begin
  process(clk)
  begin
    if (clk'event and clk = '1') then
      a <= d;
      b <= a;
      q <= b;
    end if;
  end process;
end behave;
```



How many registers?



# Variable vs. Signal Example

entity regv is

```
Port (clk,d      : in std_logic;  
      q          : out std_logic);
```

```
end regv;
```

architecture behave of regv is

```
begin
```

```
process(clk)
```

```
    variable a,b : std_logic;
```

```
begin
```

```
    if (clk'event and clk = '1') then
```

```
        a := d;
```


```
        b := a;
```

```
        q <= b;
```

```
    end if;
```

```
end process;
```

```
end behave;
```

 

How many registers?



# VHDL RULES

# One Output Per process

- This is a standard adopted by the ECTET department.
- What is an output of a process?
  - Any signal on the left hand side of an assignment statement
- The number of processes does not affect the final implementation. However ....
  - Less chance of unintentionally creating a latch
  - Higher probability that that process can be re-used in a future design

# Avoid Latches

- If a signal is assigned in one branch of a case, it must be assigned in all branches

```
bad: PROCESS (inputs) IS
  BEGIN
    CASE inputs IS
      WHEN "001" | "010" | "100" | "111" =>
        S <= '1';
      WHEN "011" | "101" | "110" | "111" =>
        Cout <= '1';
      WHEN OTHERS =>
        S <= '0';
        Cout <= '0';
    END CASE;
  END PROCESS;
END behavioral;
```

What is the problem here?

# Avoid Latches

- If a signal is assigned in one branch of if/elsif/else, it must be assigned in all branches

Bad: Process(inputs) is

Begin

if inputs = "001" then

S <= '1';

Elsif inputs = "011" then

Cout <= '1';

Else

S <= '0';

Cout <= '0';

End if;

End Process;

What is the problem here?

# Avoid Latches

- An if requires an else unless default values are assigned prior to the if/elsif/else statement

```
process(ins)
begin
  if (ins = "00") then
    y <= "11";
  elsif (ins = "10") then
    y <= "00";
  elsif (ins = "01") then
    y <= "10";
  end if;
end process;
```

What is the problem here?

# Avoid Latches

- If the same signal is on the right and the left hand sides of an assignment it must be in a synchronous (clk) process

```
process(ins)
begin
  if (ins = "00") then
    y <= "11";
  elsif (ins = "10") then
    y <= "00";
  else
    y <= y;
  end if;
end process;
```


What is the problem here?

# Avoid Latches

```

ins_sig: process (in_vect)
BEGIN
  if in_vect(1 downto 0) = "00" then
    y_ins <= "11";
  elsif in_vect(1 downto 0) = "10" then
    y_ins <= "00";
  else
    y_ins <= y_ins;
  end if;
end process;
y_bits <= y_ins;

```

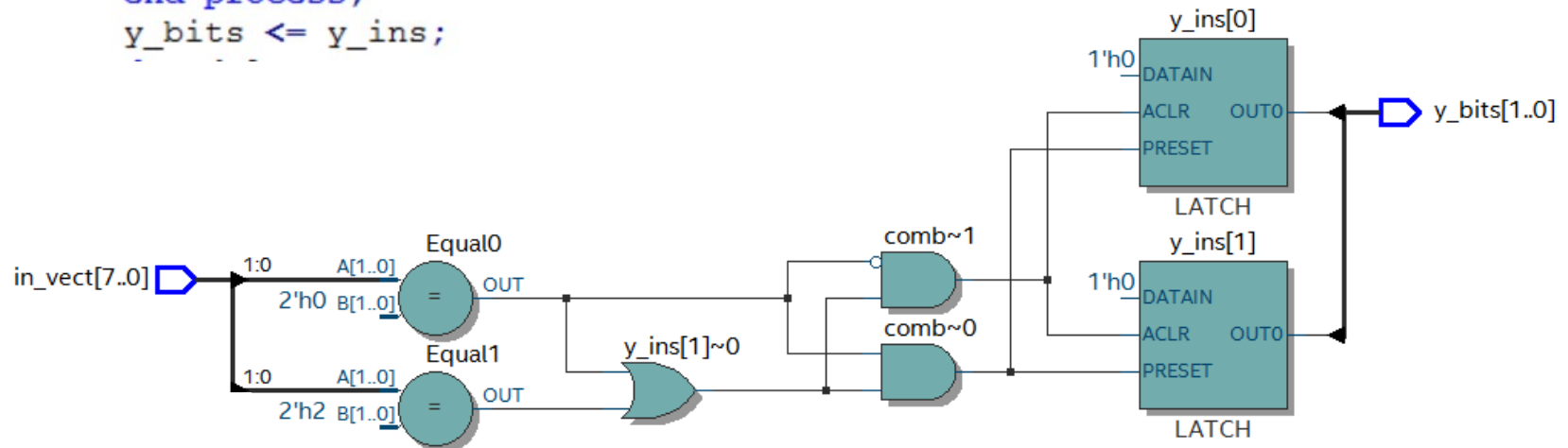



# Coding Guidelines

- From the textbook
  - Use meaningful signal names
  - Use generics when possible
  - Use `STD_LOGIC_VECTOR` for ports and cast to other types internally
  - Use descending indices (X downto Y)
  - Use the same name for project, file and entity
  - Do not use `BUFFER` type, use an internal signal instead
  - Comment your code
  - Use 3 + processes for state machines

# What is Synthesis


- Synthesis means taking a higher-level description and creating an equivalent lower-level description
  - Moving from English to VHDL, to schematic, to circuit.
  - We will focus on the creation of RTL and gate level design from VHDL

# What is RTL?


- Register-Transfer Level
- The level of abstraction in which operation is described in terms of data transfers from one register to another register and data manipulations performed combinational logic that exists between the registers

# What is RTL?

- Concerned with the flow of data

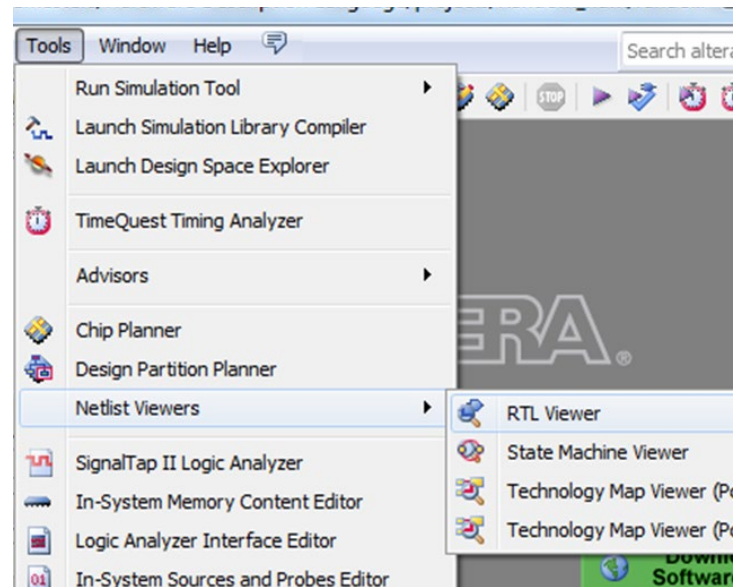

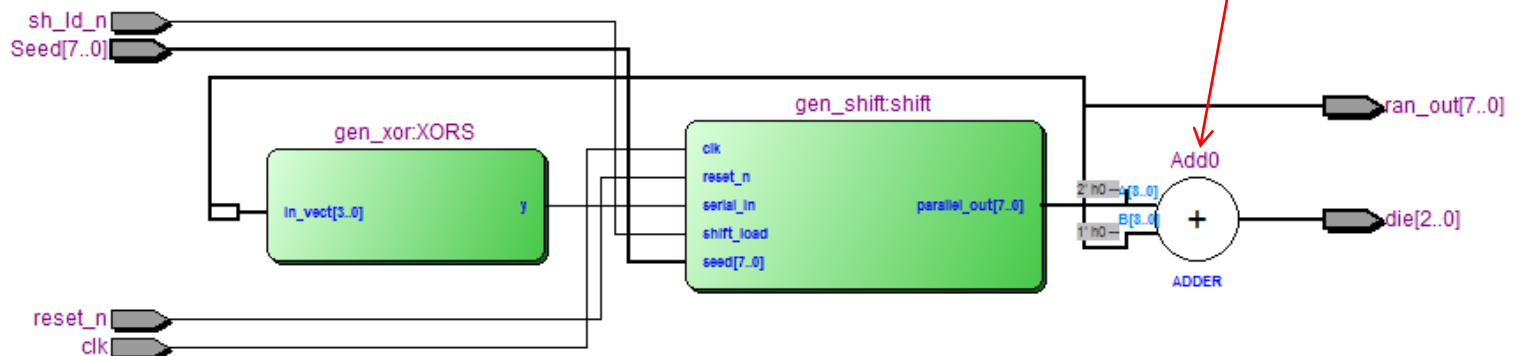Indicates addition, but  
Does not include circuitry




# Synthesis Tools


- Synthesis tools convert VHDL to RTL and gate level representation
  - The tool infers basic logic structures from the code
  - The way the code is written makes a BIG difference
 
# Synthesis Example

```
entity deeff is
  port (D, clk, reset_n : in std_logic;
        Q               : out std_logic);
end deeff;
architecture behave of deeff is
begin
  synch: process(clk, reset_n) is
  begin
    if (clk'event and clk = '1') then
      if (reset_n = '0') then
        Q <= '0';
      else
        Q <= D;
      end if;
    end if;
  end process;
end behave;
```


 
```
entity deeff is
  port (D, clk, reset_n : in std_logic;
        Q               : out std_logic);
end deeff;
architecture behave of deeff is
begin
  async: process(clk, reset_n) is
  begin
    if (reset_n = '0') then
      Q <= '0';
    elsif (clk'event and clk = '1') then
      Q <= D;
    end if;
  end process;
end behave;
```



WHY?



# Synthesis Example

```
architecture behave of mux8to1 is
begin
```

```
    process (a, b, c, d, e, f, g, h, sel) is
    begin
        case sel is
            when "000" => y <= a;
            when "001" => y <= b;
            when "010" => y <= c;
            when "011" => y <= d;
            when "100" => y <= e;
            when "101" => y <= f;
            when "110" => y <= g;
            when others => y <= h;
        end case;
    end process;
end behave;
```

```
process (a, b, c, d, e, f, g, h, sel) is
begin
```

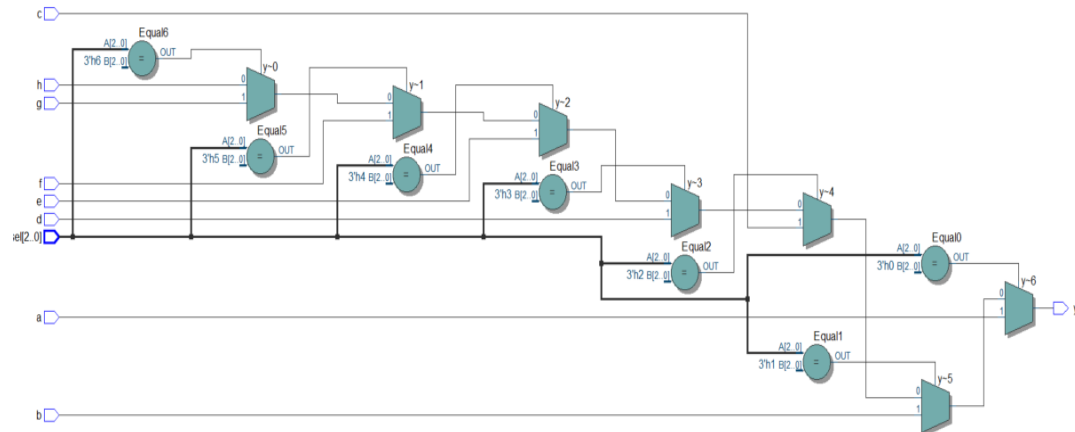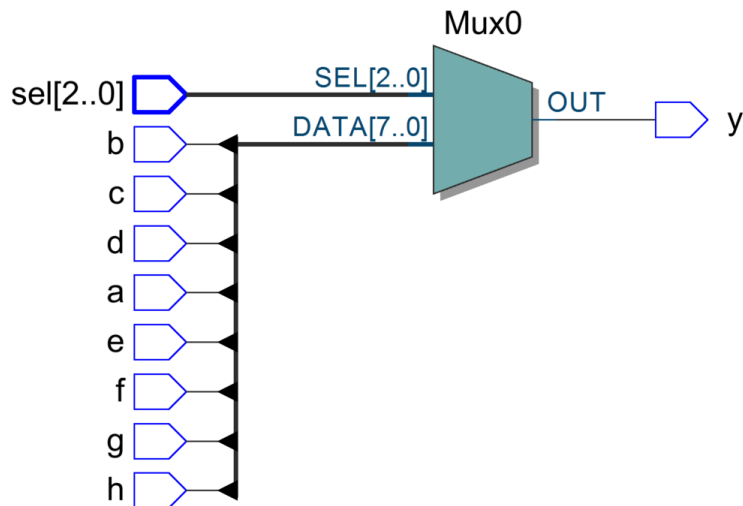
```
    if sel = "000" then y <= a;
    elsif sel = "001" then y <= b;
    elsif sel = "010" then y <= c;
    elsif sel = "011" then y <= d;
    elsif sel = "100" then y <= e;
    elsif sel = "101" then y <= f;
    elsif sel = "110" then y <= g;
    else
        y <= h;
    end if;
end process;
end behave;
```


 
# Primitive Inference

```
entity tri_state is
  port(en, A : in std_logic;
        Y : out std_logic);
end tri_state;

architecture behave of tri_state is
begin
  process (en, A) is
  begin
    if en = '1' then
      Y <= A;
    else
      Y <= 'Z';
    end if;
  end process;
end behave;
```






# Primitive inference

- RAM

```
type ram_type is array ((2**addr_width - 1) downto 0) of std_logic_vector (data_width - 1 downto 0);
signal RAM : ram_type;

begin
|process(clk)
|begin
|    if (clk'event and clk = '1') then
|        if (we = '1') then
|            RAM(to_integer(unsigned(addr))) <= d_in;
|        end if;
|    end if;
end process;
d_out <= RAM(to_integer(unsigned(addr)));
```

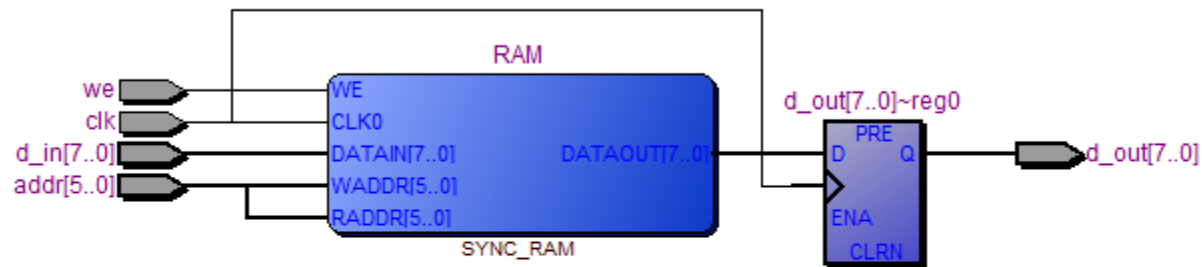


# Tools Optimize for Timing

- If the tool recognizes an implementation that is better than another, it gets inferred

- 32 bit parity detector

- Written:

 

- inferred

