



Digital Logic Review II

Announcements

- No Class next Monday
- Homework #1 due in 1 week
- Check your lab schedule in the Syllabus to see when lab reports and prelabs are due!

Group Homework

- Review homework policies
 - Posted on MyCourses
- Time for teams find each other and exchange contact info



msb		lsb		
A	B	C	D	box
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

K-map Review

		msb			
		lsb			
		$\bar{A} \bar{B}$	$\bar{A} B$	$A B$	$A \bar{B}$
$\bar{C} \bar{D}$	0	4	12	8	
$\bar{C} D$	1	5	13	9	
$C D$	3	7	15	11	
$C \bar{D}$	2	6	14	10	


K-map Review

- I. Set up the k-map for the following function and generate the simplified equation from the k-map

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Seven Segment Display Review

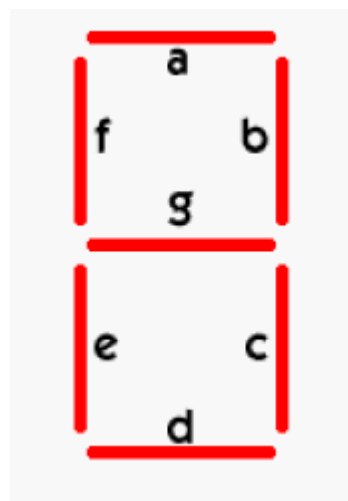- Seven Segment displays
 - Called HEX0 and HEX1 on DE0 boards



HEX00 = a

HEX01 = b

:

:


HEX06 = g

- 0 is ON : 1 is OFF
 - Called common _____?

Seven Segment Display Review

- To display 2 drive the outputs as follows:

	a	b	c	d	e	f	g
1 or 0							

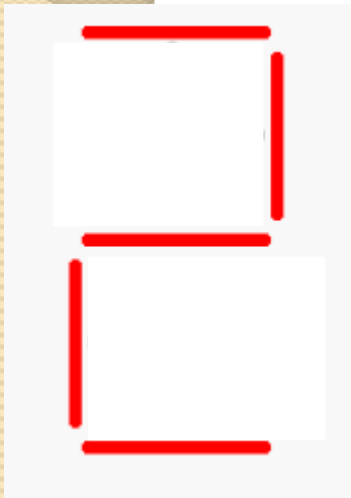


- A digital circuit that drives a seven segment display has seven outputs
 - Ergo: seven k-maps are necessary when designing

Seven Segment Display Pinout

HEX00	PIN_U21	Seven Segment Digit 0[0]
HEX01	PIN_V21	Seven Segment Digit 0[1]
HEX02	PIN_W22	Seven Segment Digit 0[2]
HEX03	PIN_W21	Seven Segment Digit 0[3]
HEX04	PIN_Y22	Seven Segment Digit 0[4]
HEX05	PIN_Y21	Seven Segment Digit 0[5]
HEX06	PIN_AA22	Seven Segment Digit 0[6]

Waveform Simulation

- Given the following circuit

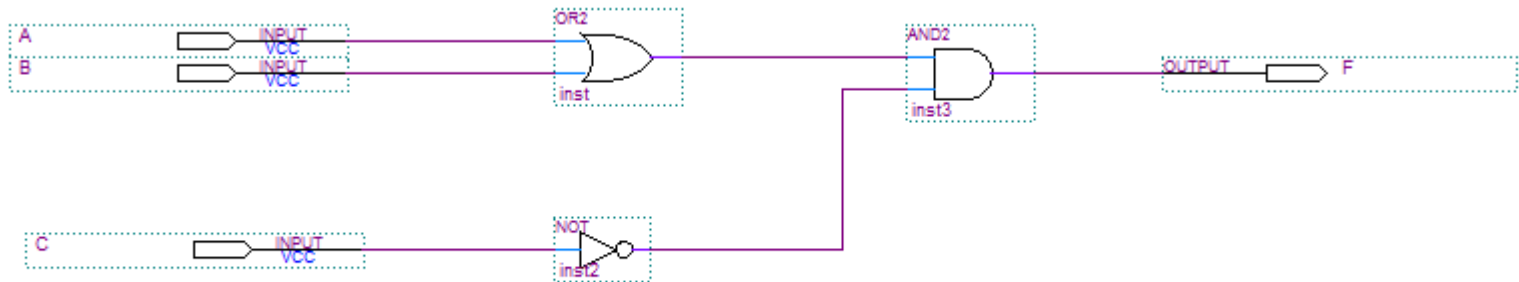


- Test every combination of A, B & C

A	B	C	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


Waveform Simulation

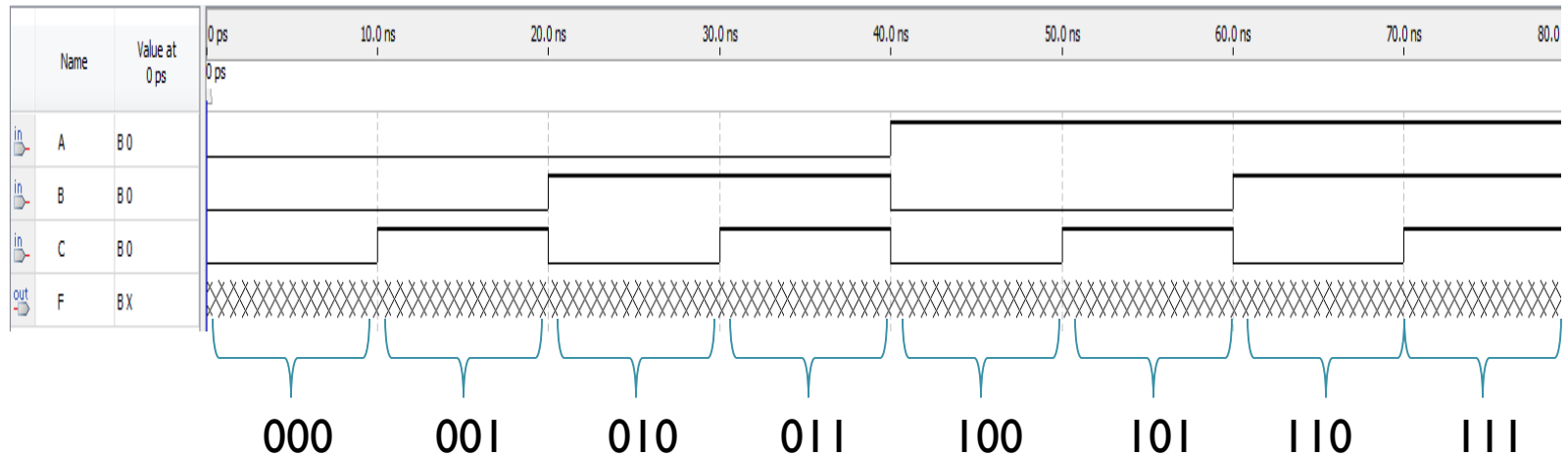- Use a waveform to test every combination




Waveform Simulation

- Run simulation tool

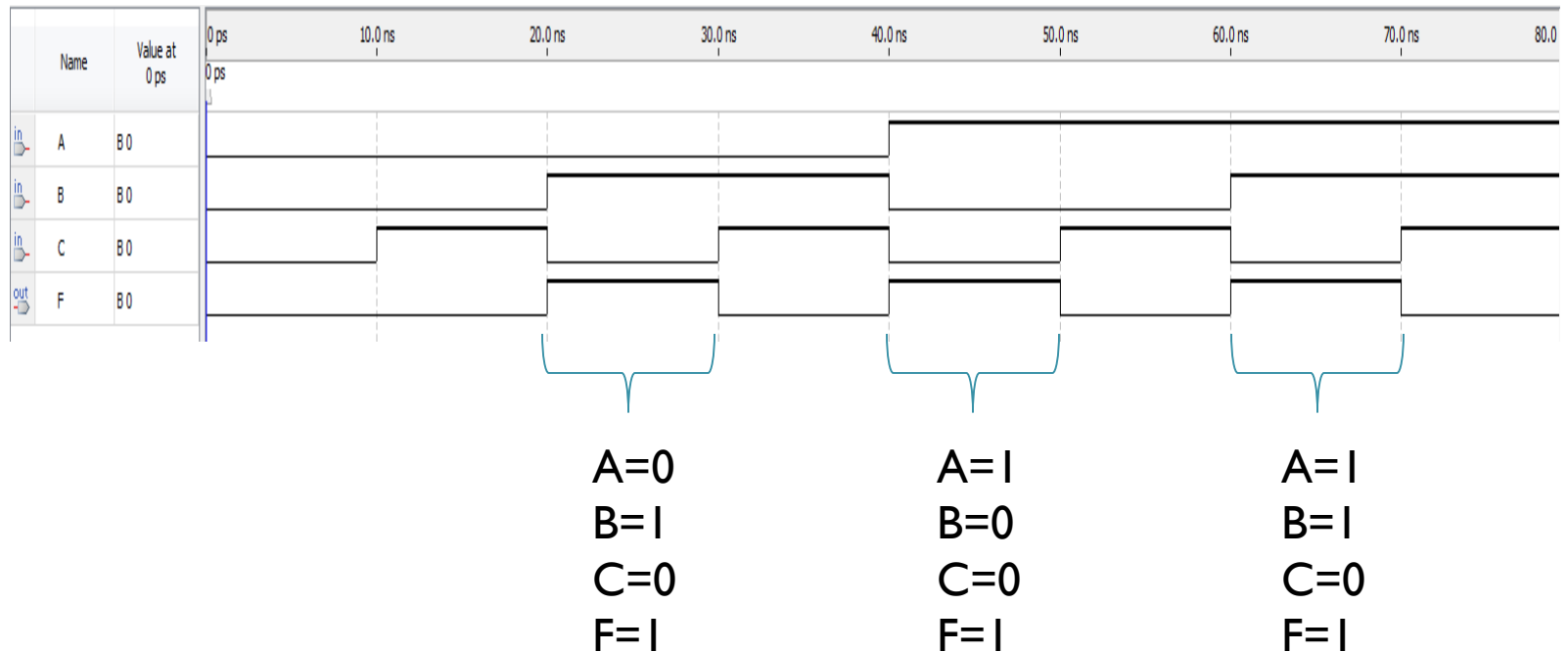

Waveform Simulation

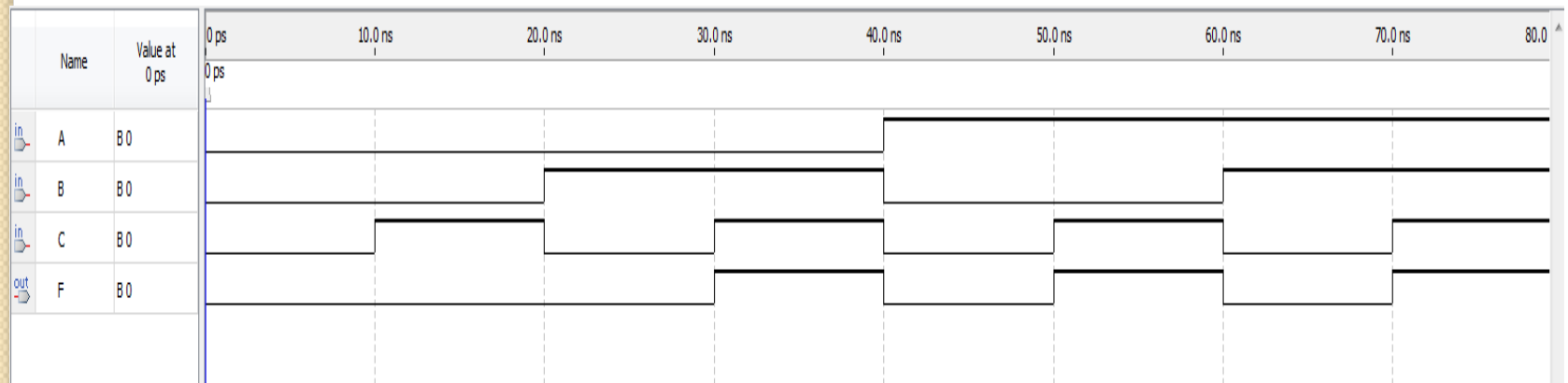- Make sure the results are what you expect



- What does the waveform for F tell you?