



Introduction to VHDL

Announcements

- Homework #1 due today
- Homework #2 is posted
- Reading Assignment
 - Ch. 1, Ch. 2 sections 1-5
- Free homework grade for attending critical thinking lecture



Join us for the 2019 Fram Signature Lecture!

“POWERFUL STUFF: An Entrepreneurial Mindset Built Upon Critical Thinking” with Doug Melton of KEEN

Date: Tuesday, September 17, 2019

Time: 3:30pm – 4:45pm

Place: Ingle Auditorium *(Reception immediately following in Fireside Lounge)*

**Access Services will be providing interpreters for this event*

Hardware Description Languages

- Hardware description language (HDL) is similar to a computer program except that it is used to describe hardware.
- Common HDLs
 - VHDL (VHSIC Hardware Description Language)
 - Verilog
 - *Both languages are easy to learn and hard to master. Once you have learned one of these languages, you will have no trouble transitioning to the other.*

VHDL History

- Developed in the mid-1980's – initiative from Department of Defense
 - Originally used for simulation and modeling
 - Synthesis tools were later developed to create logic circuits directly from VHDL behavioral descriptions

Pause for definitions

- Simulation

- A testing procedure to ensure that the circuit you have designed functions correctly.
 - Force 1's and 0's into the circuit and observe the outputs for correctness
 - Can be done with waveforms or written in VHDL


- Synthesis

- Translation of a source code into a hardware structure that implements the intended functionality
 - Simply put: turning a written description into underlying gates

VHDL Module Structure

- A VHDL module consists of an Entity and an Architecture
 - The entity describes the **ports** of the module
 - The direction of all I/O signals
 - The types of all I/O signals
 - The architecture describes the **functionality** of the module
 - The internal structure of the module
 - The behavior of the module

VHDL Module Structure

 

Text file (mydesign.vhd)

Example of VHDL Module

- 3 sections
- File extension is .vhd
- Name of file is usually the entity name

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

Library Declaration

```
ENTITY nand_gate IS  
    PORT( a      : IN STD_LOGIC;  
          b      : IN STD_LOGIC;  
          z      : OUT STD_LOGIC);  
END nand_gate;
```


Entity

```
ARCHITECTURE model OF nand_gate IS  
BEGIN  
    z <= a NAND b;  
END model;
```

Architecture


Entity Declaration

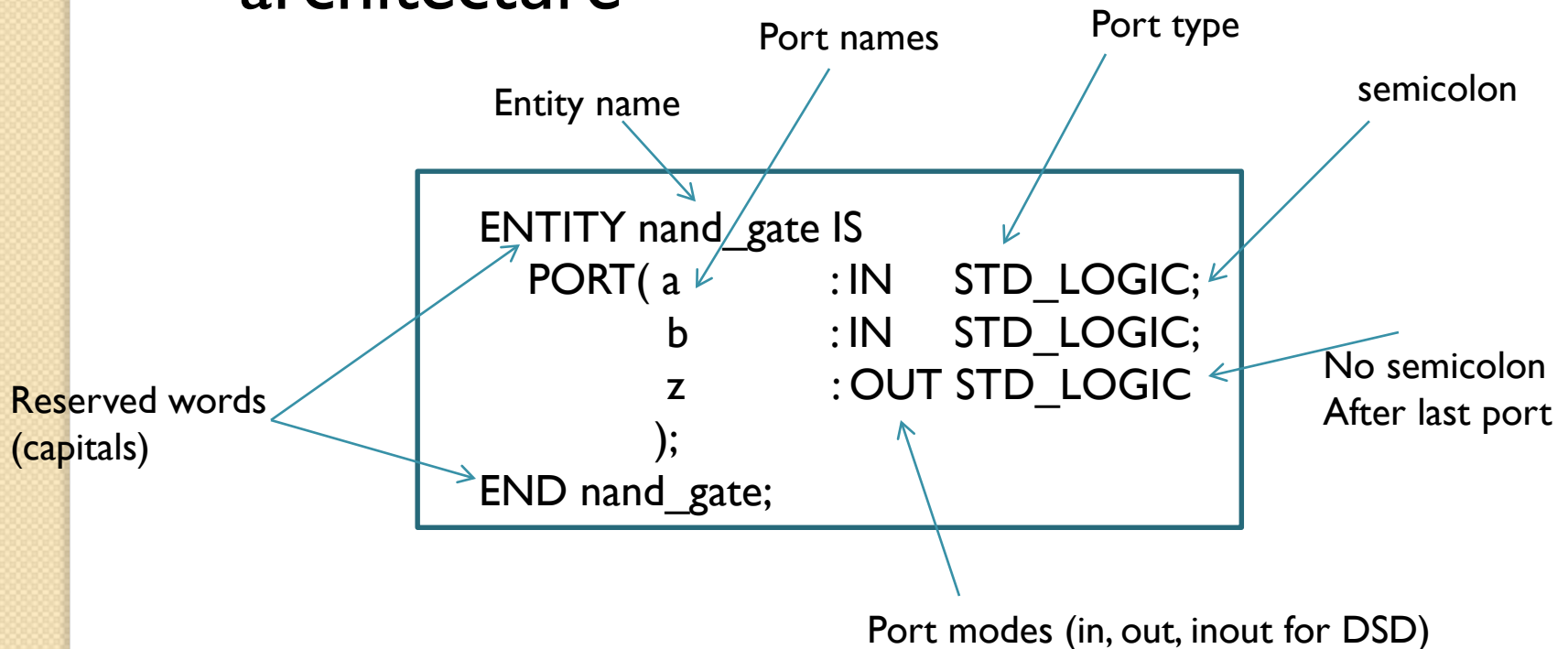- Describes the interface of the component
- Thought of as a wrapper that exposes only external interfaces for the architecture




Entity Declaration

 - Write the entity declaration for the following 'black box'




Architecture Definition

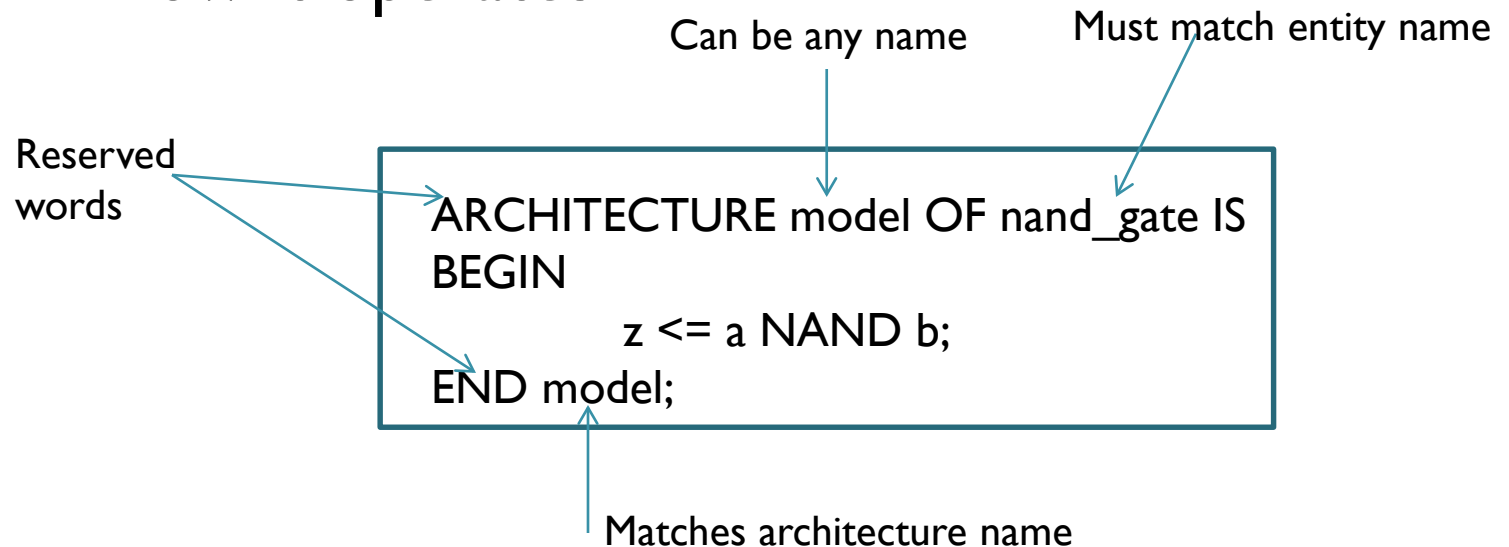- Architecture describes functionality of the module
 - Structural – describes the system in terms of how it is built
 - Behavioral – describes the system in terms of how it operates




Architecture Definition

 - Using AND, NOT and OR write the architecture for the circuit below




```
ENTITY example IS
    PORT( a,b,c      :IN   STD_LOGIC;
          z          :OUT  STD_LOGIC);
END example;
```

Write the VHDL for the following

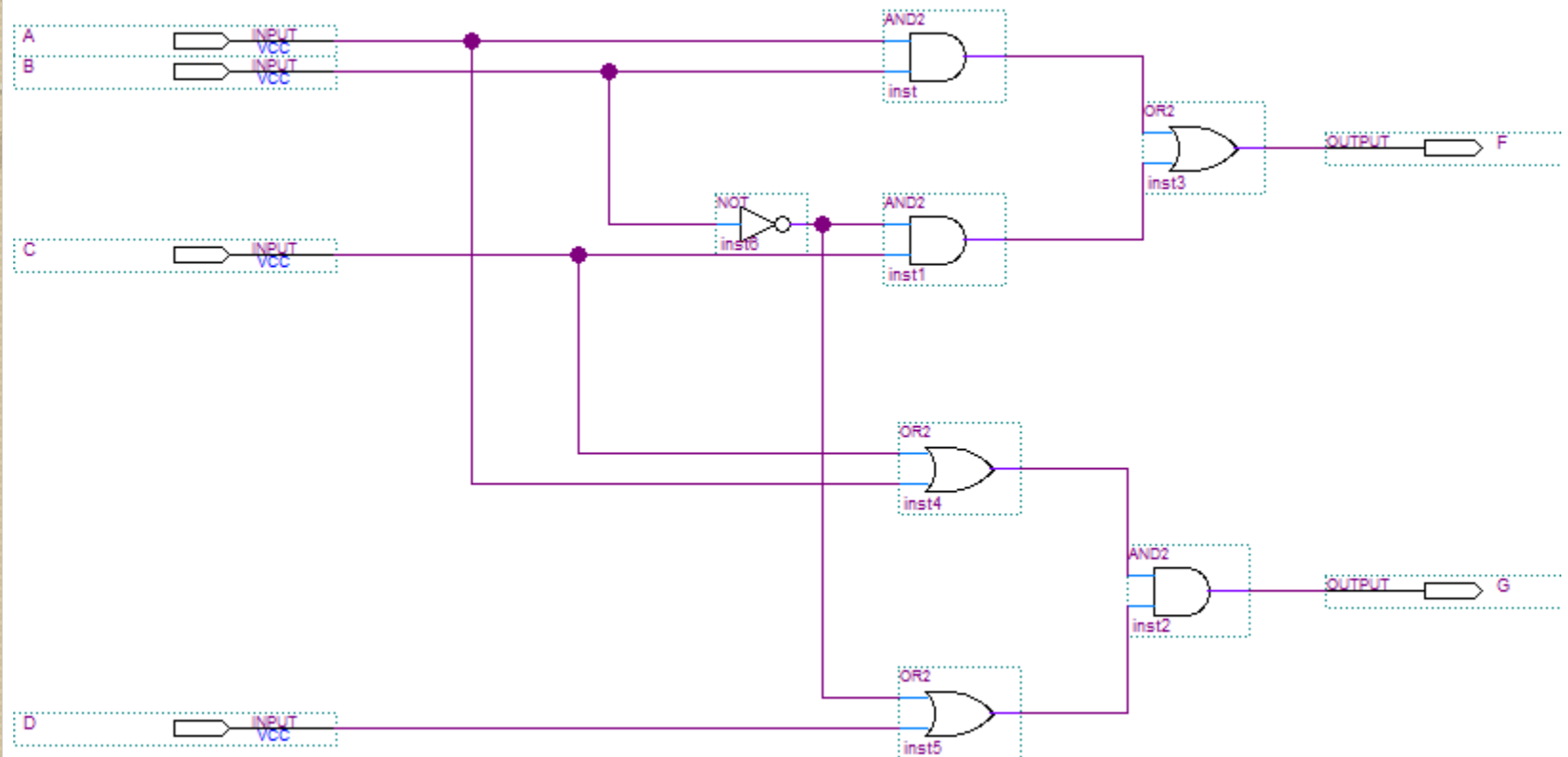



Now Consider This

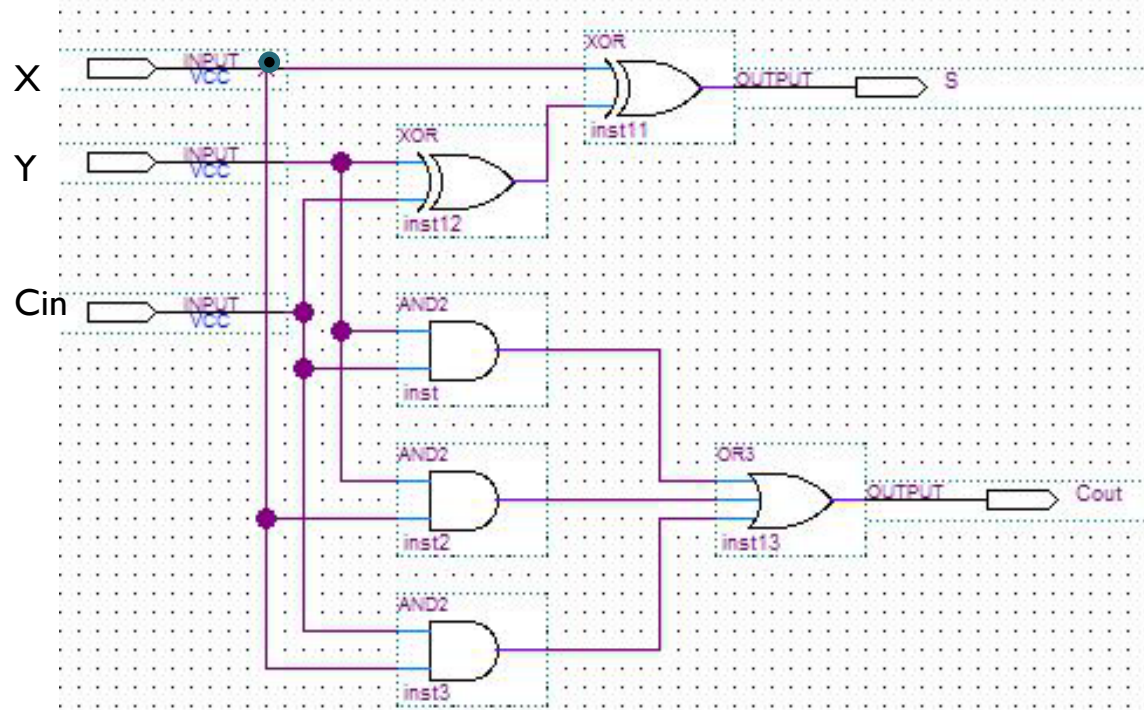

ENTITY fulladd IS

PORT(Cin,X,Y : IN STD_LOGIC;
S, Cout : OUT STD_LOGIC);

END fulladd;

ARCHITECTURE structural OF fulladd IS

BEGIN

S <= X XOR (Y XOR Cin);

Cout <= (X AND Y) OR (X AND Cin) OR (Y AND Cin);

END structural;

VHDL for full adder

- Problem with previous example is that equations get long
- A better way to write it is to use signals
- Signals are declared after the ARCHITECTURE line but before the BEGIN
- Signals represent internal wires and busses in the design

Full Adder Arch. with signals

ENTITY fulladd IS

PORT(Cin, X,Y : IN STD_LOGIC;
 S, Cout : OUT STD_LOGIC);

END fulladd;

Entity is the same

ARCHITECTURE structural OF fulladd IS

SIGNAL xor1, and1, and2, and3 : STD_LOGIC;

BEGIN

xor1 <= Y XOR Cin;

and1 <= Y AND Cin;

and2 <= Y AND X;

and3 <= X AND Cin;

S <= X XOR xor1;

Cout <= and1 OR and2 OR and3;

END structural;