



MSI – Medium Scale Integration

From traditional gate designs to VHDL

Announcements

- HW #6 due today
- HW #7 posted – new homework groups
 - Extended dropbox due date due to long weekend
- Oct 21st Exam #2

New Homework Groups

- Exchange contact information

Group 1			Group 2			Group 3			Group 4		
Smith,Marco			Klino,Justin			Orozco,Julian			MacDougall,Skyler		
Aguilar,Christian			Towler,Amauri			Sullivan, Dea			Dardis,TJ		
Ferguson, Ken			Berens,Peter			Wurz,Cole			Fisher,Dustin		
Group 5			Group 6			Group 7			Group 8		
Valla,Nathaniel			DeMartino,Lenny			Adachi,Shogo			Yang,Calvin		
Bhattarai,Sushil			Dobmeier,Zach			Lin,Vivian			Alam,Tanveer		
Abdallah,Baha			Polley,Joe			Ho,Jessica			Barraza,Nathan		
Group 9			Group 10			Group 11			Group 12		
Louie,Corey			Chan,Samir			Chung,Elaina			Yang,Zhentao		
Davidson,Seth			Cabrera,Vincent			Somers,Connor			Heineman,Hunter		
Southwell,Isaac			Afriyie,Naa			Berntson,Steve			Dickey,Kevin		
Group 13									Orpiano,Jhay		
			Kotlo,Shavan								
			Serra,Andrew								
			Tuttle,Dallas								

Comparators

- Compare two binary strings or words
- Digital comparator
- Compare bit-by-bit

VHDL Comparator

compare_8b.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY compare_8b IS
    PORT(a, b          : IN  std_logic_vector(7 DOWNTO 0);
         agb, aeb, alb : OUT  std_logic);
END compare_8b;

ARCHITECTURE arc OF compare_8b IS
    SIGNAL result : std_logic_vector(2 DOWNTO 0);
BEGIN
    PROCESS (a,b)
    BEGIN
        IF a<b THEN
            result <= "001";
        ELSIF a=b THEN
            result <= "010";
        ELSIF a>b THEN
            result <= "100";
        ELSE
            result <= "000";
        END IF;
        agb <= result(2);
        aeb <= result(1);
        alb <= result(0);
    END PROCESS;
END arc;
    
```

Sensitivity list (points to (a,b) in PROCESS)

3-bit internal SIGNAL result (points to result signal declaration)

Assign vector elements to outputs (points to agb, aeb, alb assignments)

compare_8b.vhd

compare_8b

inst

Diagram illustrating the VHDL code for an 8-bit comparator (compare_8b.vhd) and its corresponding block diagram.

The code defines an ENTITY `compare_8b` with two 8-bit input vectors `a` and `b`, and three single-bit output signals `agb`, `aeb`, and `alb`. The ARCHITECTURE `arc` implements the logic using a PROCESS block.

The PROCESS block has a sensitivity list `(a,b)`. It uses IF-THEN-ELSE and ELSIF logic to compare the inputs:

- IF `a < b` THEN `result <= "001";`
- ELSIF `a = b` THEN `result <= "010";`
- ELSIF `a > b` THEN `result <= "100";`
- ELSE `result <= "000";`

The 3-bit internal SIGNAL `result` is then assigned to the outputs:

- `agb <= result(2);`
- `aeb <= result(1);`
- `alb <= result(0);`

The block diagram shows the `compare_8b` component (inst) with inputs `a[7..0]` and `b[7..0]`, and outputs `agb`, `aeb`, and `alb`.

Synthesized Comparators

- Every time a relational statement is included in VHDL, a comparator is synthesized.
- Examples
 - If (var1 >= 1)
 - If (var1 = 0)
 - If (var1 < var2)
- Note, less hardware is inferred with = than <, >, <=, /=, or >=
 - Use the = case if possible

Synthesized Comparators

IF (var l = 0) then

 x <= '1';

ELSE

 x <= '0';

END IF;

Even though the result is the same,
This method is better

IF (var l >= 1) then

 x <= '0';

ELSE


 x <= '1';

END IF

*Assume var l is an unsigned number

Decoding

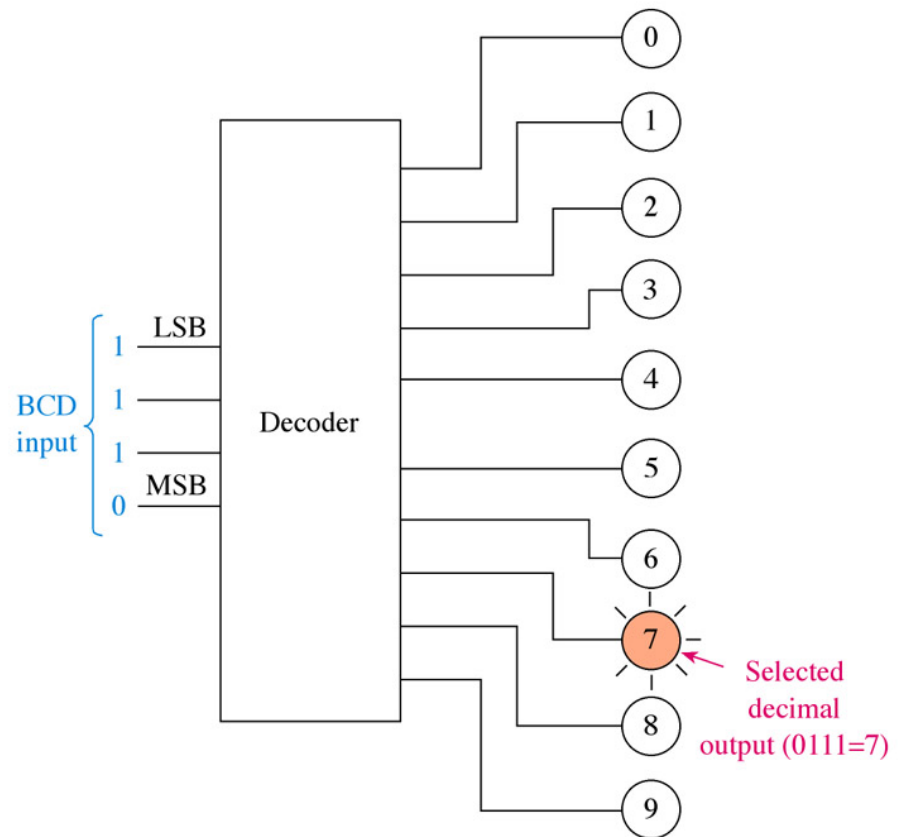- Process of converting some code (binary, BCD, or hex) to a single output
 - One and only one output active at a time
- 4-bit BCD decoder
 - Comprised of a combination of logic gates



Decoding

- 3 to 8 Decoder Truth Tables

TABLE 8-1

Truth Tables for an Octal Decoder

(a) Active-HIGH Outputs

Input			Output							
2^2	2^1	2^0	0	1	2	3	4	5	6	7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Note: The selected output goes HIGH.

(b) Active-LOW Outputs

Input			Output							
2^2	2^1	2^0	0	1	2	3	4	5	6	7
0	0	0	0	1	1	1	1	1	1	1
0	0	1	1	0	1	1	1	1	1	1
0	1	0	1	1	0	1	1	1	1	1
0	1	1	1	1	1	0	1	1	1	1
1	0	0	1	1	1	1	0	1	1	1
1	0	1	1	1	1	1	1	0	1	1
1	1	0	1	1	1	1	1	1	0	1
1	1	1	1	1	1	1	1	1	1	0


Note: The selected output goes LOW.

Encoding

- Opposite of decoding
- Used to generate a coded output from a singular active numeric input line.

Encoding

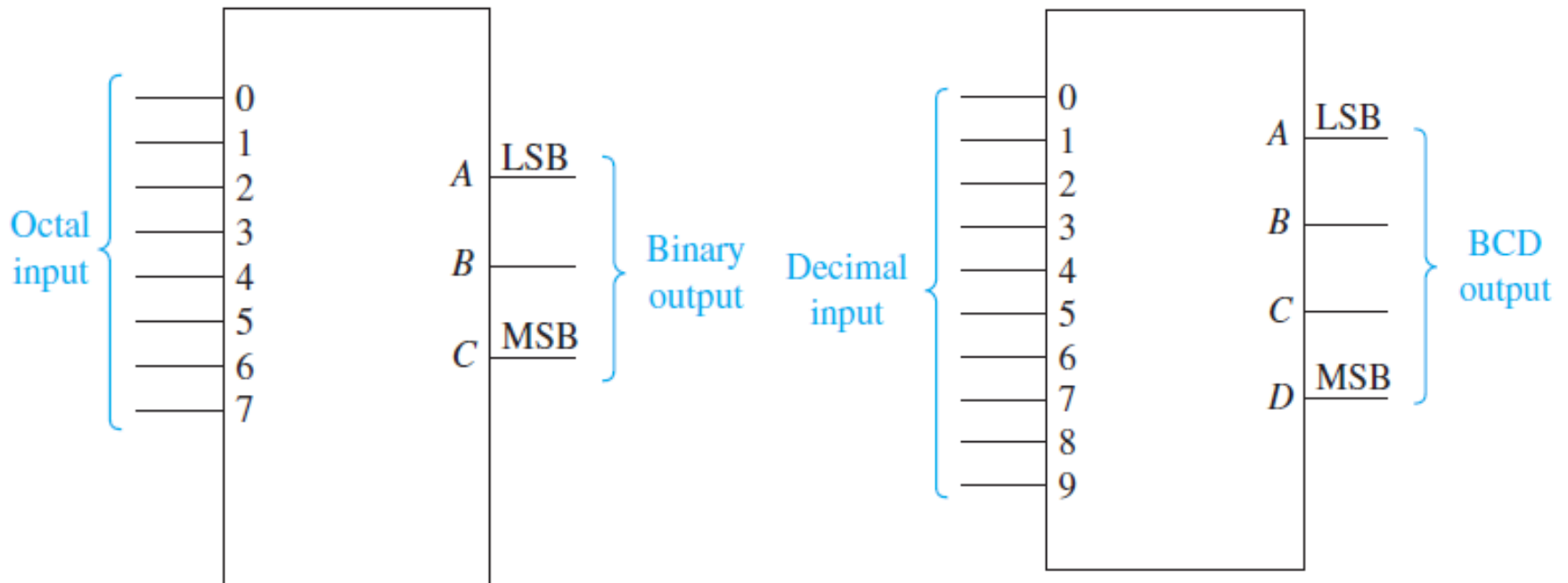- Octal-to-binary and decimal-to-BCD encoders



- Only 1 input active at a time

VHDL Octal Priority Encoder


```
ENTITY encode8 IS
    PORT ( Ins  : in  STD_LOGIC_VECTOR(7 downto 0);
          Outs : out  STD_LOGIC_VECTOR(2 downto 0));
END encode8;

ARCHITECTURE priority OF encode8 IS
    BEGIN
        PROCESS (Ins)
            BEGIN
                IF Ins(7) = '1' then
                    Outs <= "111";
                ELSIF Ins(6) = '1' then
                    Outs <= "110";
                ELSIF Ins(5) = '1' then
                    Outs <= "101";
                ELSIF Ins(4) = '1' then
                    Outs <= "100";
                ELSIF Ins(3) = '1' then
                    Outs <= "011";
                ELSIF Ins(2) = '1' then
                    Outs <= "010";
                ELSIF Ins(1) = '1' then
                    Outs <= "001";
                ELSE
                    Outs <= "000";
                END IF;
            END PROCESS;
        END priority;
END priority;
```

What happens if more than one input is active?


Code Converters

 - Convert a coded input into another form
- Hexadecimal to seven segment display is an example you are familiar with



Multiplexers

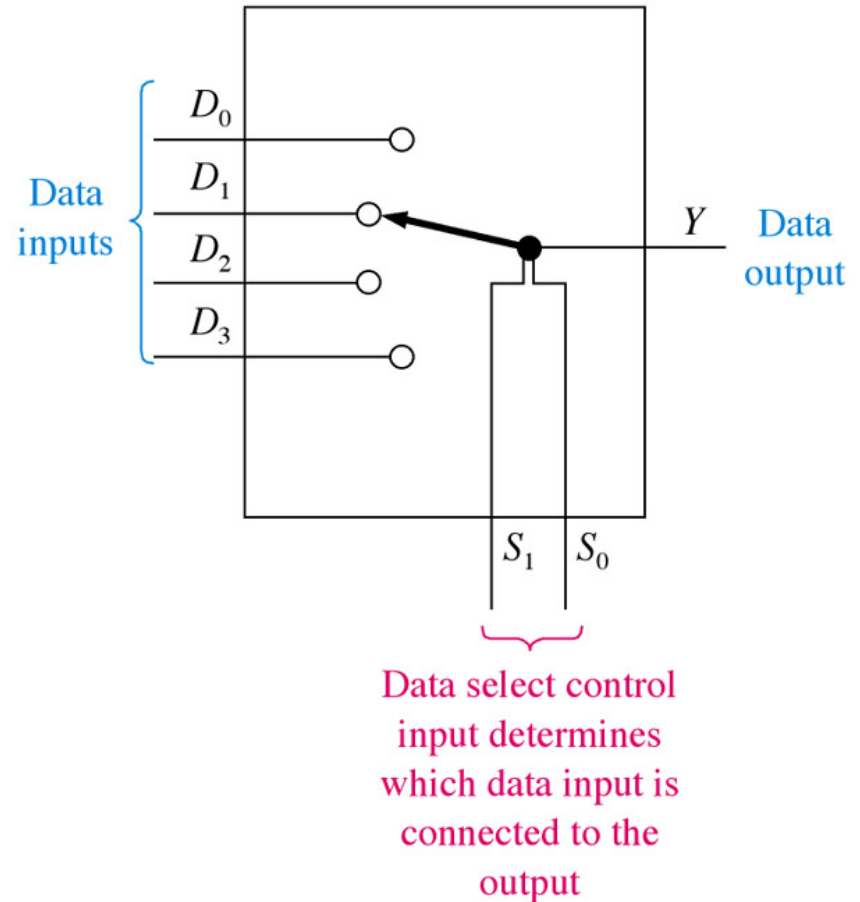- Funneling several data lines into a single one for transmission to another point
- Data select control determines which input is transmitted



Multiplexer sizes

- Common Sizes
 - 4-to-1 (2 select lines)
 - 8-to-1 (3 select lines)
 - 16-to-1 (4 select lines)
- Pattern?
 - For n-to-1 mux, $\log_2(n)$ select lines needed

Mux / Case statement

- A case statement synthesizes to a Mux

Choose : process(a,b,c,d,en)

Begin

case (en) is

when "00" => out <= a;


when "01" => out <= b;

when "10" => out <= c;

when others => out <= d;

end case;

End process;

 

Case vs. IF-THEN-ELSE

architecture behave of mux8to1 is
begin

```



process (a, b, c, d, e, f, g, h, sel) is
begin
  case sel is
    when "000" => y <= a;
    when "001" => y <= b;
    when "010" => y <= c;
    when "011" => y <= d;
    when "100" => y <= e;
    when "101" => y <= f;
    when "110" => y <= g;
    when others => y <= h;
  end case;
end process;
end behave;

```

```

process (a, b, c, d, e, f, g, h, sel) is
begin
  if sel = "000" then y <= a;
  elsif sel = "001" then y <= b;
  elsif sel = "010" then y <= c;
  elsif sel = "011" then y <= d;
  elsif sel = "100" then y <= e;
  elsif sel = "101" then y <= f;
  elsif sel = "110" then y <= g;
  else
    y <= h;
  end if;
end process;
end behave;

```

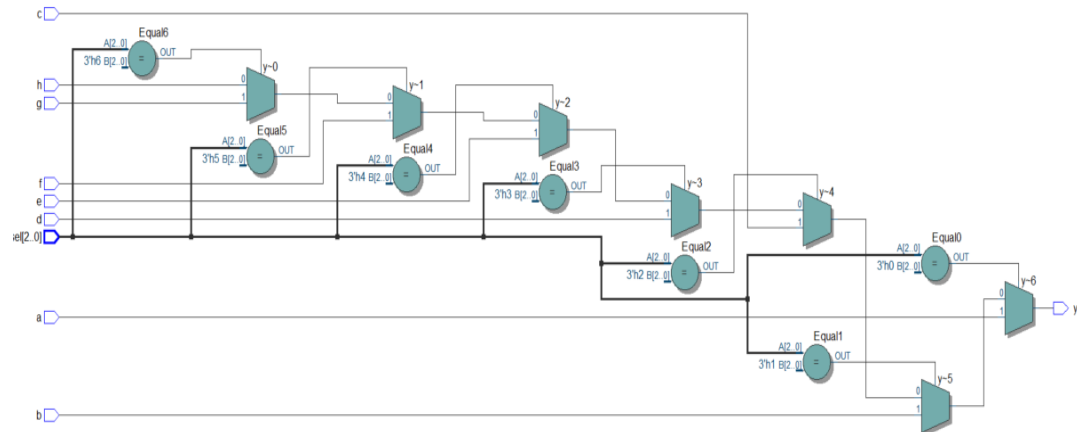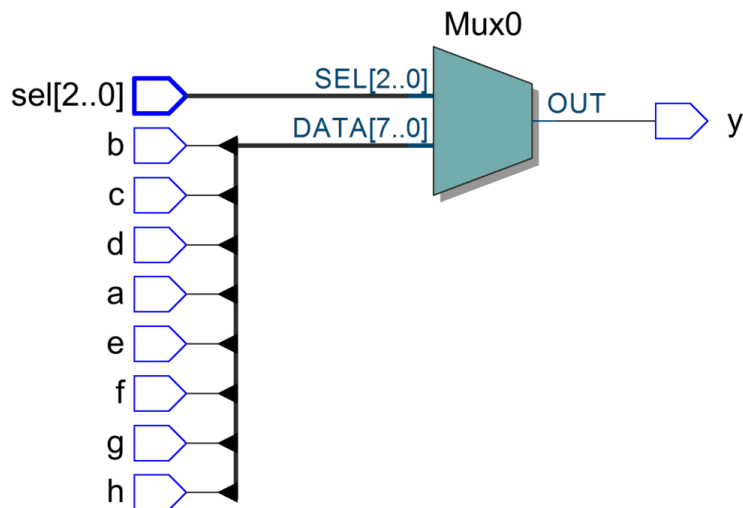

Case vs. IF-ELSIF-ELSE

- Case creates a MUX
 - One logic level regardless of # of conditions
- IF-ELSIF-ELSE creates a *priority encoder*
 - # of logic levels = # of conditions - 1
 - Why could this be a problem?