



# VHDL Registers and Counters

# Announcements


- Homework #8 posted – due Wednesday
- Quiz Wednesday on homework
- Reading assignment:
  - Chapter 6 – especially the examples

# Multibit Registers


- A D flip-flop is a 1-bit register
- Two or more D flip-flops with their clocks inputs connected together form a multibit register (aka a register)
- The width of the register is determined by the number of memory elements it contains
- Widths of 8, 16, 32 and 64 are common in computing systems
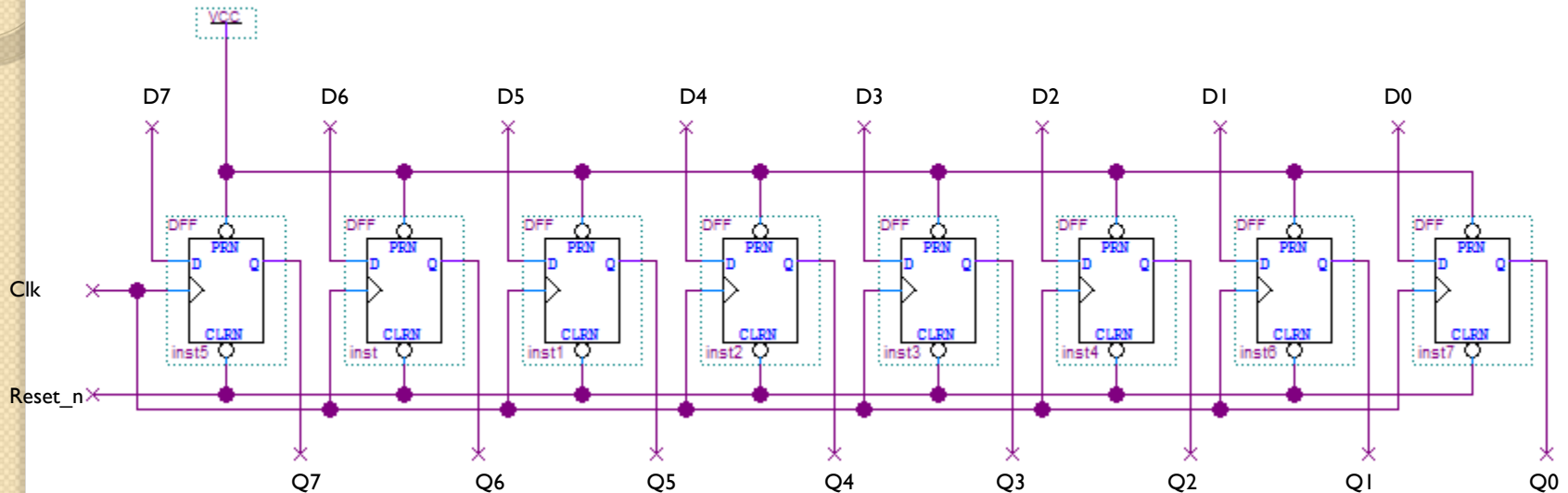
# Register VHDL

- Write the entity and architecture for an 8-bit register with asynchronous reset




# JK Flip-Flop

 

J	K	Clk	Q	QN	
0	0	↑	Q	QN	Stay the same
0	1	↑	0	1	Clear
1	0	↑	1	0	Set
1	1	↑	$\bar{Q}$	$\overline{QN}$	toggle

# Counter using JK-flip flop

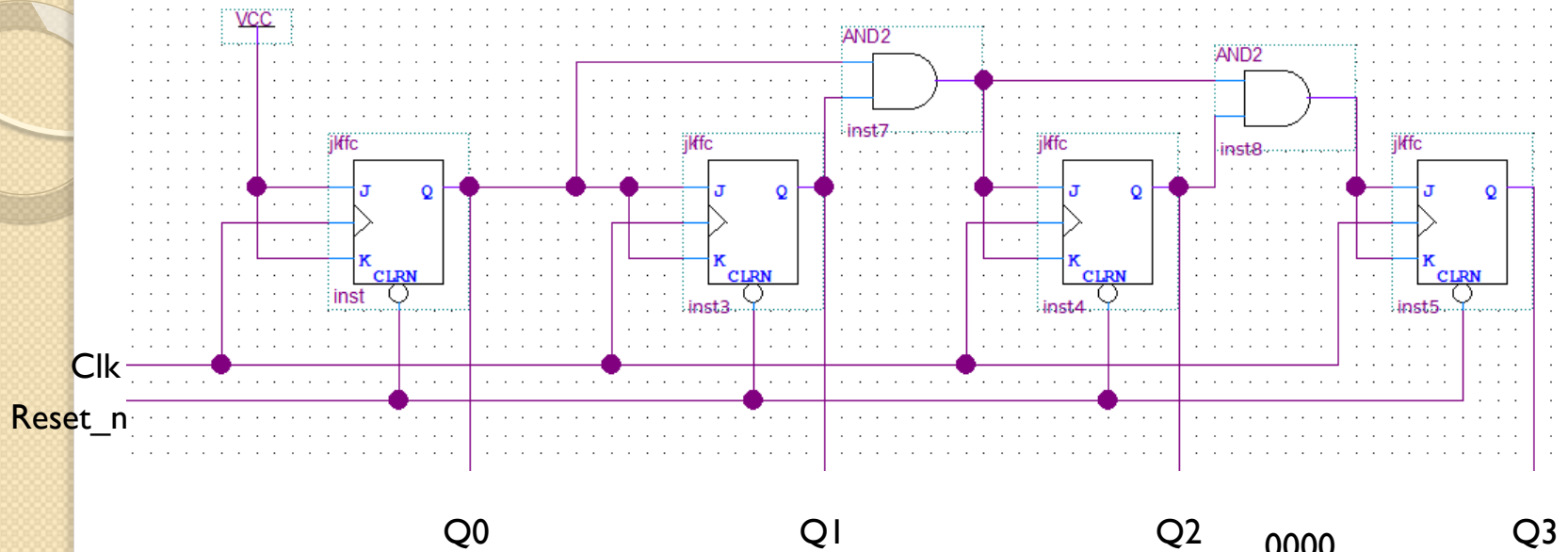

- Q0 (Least significant bit) will toggle on every clock cycle because its J and K inputs are tied to VCC
- Subsequent bits will only toggle when **all** previous Qs are 1. This is the purpose of the AND gates

Q0 Q1 Q2 Q3

0000

0001

0010

0011

0100

0101

0110

0111

1000

:

# Counters

- Simple

ENTITY Count4 IS

    PORT(clk, reset\_n : IN STD\_LOGIC;

            count      : OUT STD\_LOGIC\_VECTOR(3 downto 0));

END Count 4;

ARCHITECTURE model of Count4 IS

    SIGNAL int\_count : STD\_LOGIC\_VECTOR(3 downto 0);

BEGIN

    Simple : PROCESS(clk, reset\_n)

        BEGIN

            IF (reset\_n = '0') THEN

                int\_count <= "0000";

            ELSIF (rising\_edge(clk)) THEN

                int\_count <= int\_count + 1;

            END IF;

        END PROCESS;

        count <= int\_count;

END model;

# Counters

- Counters are commonly used for timers and clock dividers
- Always use a synchronous counter
- Ripple counters (where one stage clocks the next stage) use less gates, but produce too much delay for today's applications and clock speeds



# Counters

- Stop before rolling over

ARCHITECTURE model of Count4 IS

SIGNAL int\_count : STD\_LOGIC\_VECTOR(3 downto 0);

CONSTANT MAX\_VAL : STD\_LOGIC\_VECTOR(3 downto 0) := "1100";

BEGIN

Simple : PROCESS(clk, reset\_n)

BEGIN

IF (reset\_n = '0') THEN

int\_count <= "0000";

ELSIF (rising\_edge(clk)) THEN

IF (int\_count = MAX\_VAL) THEN

int\_count <= "0000";

ELSE

int\_count <= int\_count + 1;

END IF;

END IF;

END PROCESS;

count <= int\_count;

END model;

# Using a counter to make a timer

- The clock on the DE0 board is 50 MHz
  - How do you use that to make a  $\frac{1}{2}$  second timer?
  - How many bits would you need?

$\frac{1}{2}$  second delay = 500 ms

We need to count the number of 50 MHz clock cycles in 500 ms

50MHz clock has a period of 20 ns

# counts = delay / clock period

# counts =  $500 \times 10^{-3} / 20 \times 10^{-9} = 25 \times 10^6$

$25 \times 10^6 = 17D7840_H$

\*Don't forget to subtract 1 since we start at 0

```

ENTITY delay_unit IS
    PORT(clk, reset_n          : IN STD_LOGIC;
          flag                  : OUT STD_LOGIC); --this flag is raised every 500ms
END delay_unit;

ARCHITECTURE behave of delay_unit IS
    signal count : std_logic_vector(27 downto 0);
    constant half_sec_count : std_logic_vector(27 downto 0) := x"17D783F";
BEGIN
    PROCESS(clk, reset_n) IS
        BEGIN
            if (reset_n = '0') then                --asynchronous reset
                count <= (others => '0');
            elsif (clk'event and clk = '1') then
                if (count = half_sec_count) then    --stop when you reach 1/2 sec
                    count <= (others => '0');
                else
                    count <= count + 1;
                end if;
            end if;
        end process;
    PROCESS(clk, reset_n) IS --this process produces a 1 clk cycle flag every
        --half second.
        BEGIN
            if (reset_n = '0') then
                flag <= '0';
            elsif (clk'event and clk = '1') then
                if (count = half_sec_count) then
                    flag <= '1';
                else
                    flag <= '0';
                end if;
            end if;
        end process;
    end behave;

```

# Using an enable signal

- Within a clocked process, if you only want something to happen when a certain condition exists
  - Do not gate with clock signal
  - Use an enable

```
IF (rising_edge(clk)) THEN
```

```
  IF enable = '1' THEN
```


```
    do something;
```

```
  ELSE
```

```
    stay the same;
```
 
# Using an enable signal

- The only thing that goes in the clock line is the clock
  - **If (rising\_edge(clk)) then or**
  - **if (clk'event and clk='1') then**
- Including the enable creates a gate
  - **If (rising\_edge(clk) and enable = '1') then**



- Why is this bad?

# Using an enable signal

Begin

If reset\_n = '0' then

Q <= '0';

Elsif rising\_edge(clk) then

If enable = '1' then


Q <= D;

End if;

End if;

End process;

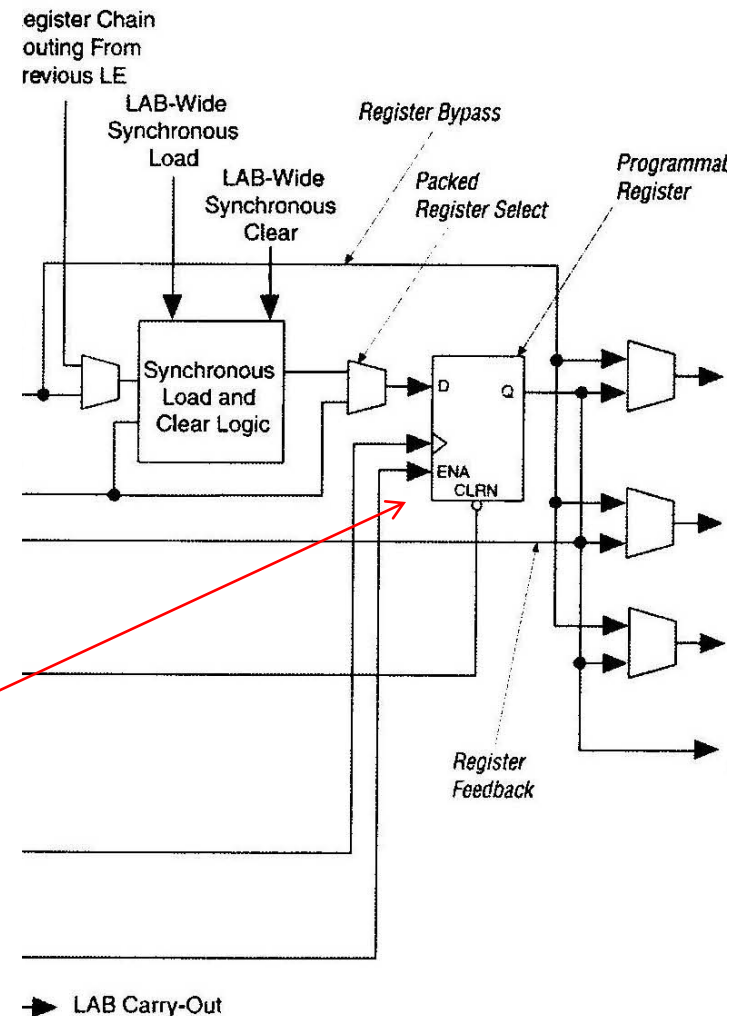Flip-flop in the cyclone II  
Is designed with enable



# BCD Counter


- Binary Coded Decimal is a 4 bit code.
  - Used to display decimal digits
  - Counting order
    - One digit: 0,1,2,3,4,5,6,7,8,9,0.....
    - Two digits: ....20,21,22,23,24,25,26,27,28,29,30...
  - Follows regular decimal counting order
    - However, each digit is represented by 4 bits

0001 1001 1001 = 199

0010 0000 0000 = 200

- A BCD counter needs to know to roll over at 1001, not 1111

# BCD Counter

 



# BCD Counter

- Starting with LSD (the least significant digit), check if it will roll over. If it rolls over, check if it causes next bit to roll over, etc...
- If no roll over, just increment

```
if (reset_n = '0') then
    BCD0 <= "0000";
    BCD1 <= "0000";
    BCD2 <= "0000";
elsif ((clk'EVENT) and (clk = '1')) then
    if BCD0 = "1001" then
        BCD0 <= "0000";
        if BCD1 = "1001" then
            BCD1 <= "0000";
            if BCD2 = "1001" then
                BCD2 <= "0000";
            else
                BCD2 <= BCD2 + 1;
            end if;
        else
            BCD1 <= BCD1 + 1;
        end if;
    else
        BCD0 <= BCD0 + 1;
    end if;
end if;
```