



Synchronous VHDL and DFF


Announcements

- No homework due this week
- HW#8 is posted
- Reminder:
 - You have to pass lab to pass the course
 - Many students did not submit a report for labs 2-4
 - Even if you do not submit a report, you need to submit your signoff sheet
- Reading assignment:
 - Ch. 6 section 2

Synchronous VHDL

- Up until this point all VHDL has resulted in combinatorial circuitry
 - What is the characteristic of combinatorial logic?
- Combinational logic has limited application in digital systems
 - Almost all digital systems are synchronous
 - What is the characteristic of synchronous logic?


Synchronous System

 

- The logic between synchronous stages is combinational
- On the clock edge the output from the combinational stages is latched (or stored) in the synchronous logic (registers)

Flip – Flop

 - Basic memory element
- Has two states; 0 or 1
- Needs a clock edge or a non-synchronous preset or clear signal to change states
- Flip – Flops are interconnected to form memory structures that store multiple bits of information as a unit



VHDL clock signal

- Synchronous elements need a clock signal for a state change
 - Should be put in an If statement within a process
 - Must be in the sensitivity list
 - Clock and Reset are only signals in sensitivity list for a clocked process
 - If a clocked process is sensitive to any other signal, it is written incorrectly

Clock Signal (con't)

- Two ways to write
 - IF (clk'EVENT) AND (clk='1') THEN
 - This is a clock signal named clk that is active on the rising edge
 - Can be used with data type BIT and STD_LOGIC
 - IF (RISING_EDGE(clk)) THEN
 - Can only be used with STD_LOGIC

Reset Signals

- All clocked elements in a system should have a reset signal
 - Why?
 - Reset can put device in '1' or '0' state
 - Can be active high or active low
- Two types of reset

Two types of Reset

- Asynchronous – reset independent of clock

ex: PROCESS(clk, reset_n) IS

BEGIN

IF (reset_n = '0') THEN

state <= '0'

ELSIF (RISING_EDGE(clk)) THEN

state <= <clocked value>;

END IF;

END PROCESS;

- Synchronous – Reset only occurs on clock edge

ex: PROCESS(clk)

BEGIN

IF (RISING_EDGE(clk)) THEN

IF (reset_n = '0') THEN

state <= '0';

ELSE

state <= <clocked value>;

END IF;

END IF;

END PROCESS;


} Nested If

Important To Remember

- In Asynchronous
 - Reset condition is the IF
 - Clock condition is the ELSIF
 - NO ELSE
 - All logic is nested under elseif
- In Synchronous
 - Clock condition is the IF
 - NO ELSE to go with the clock's IF
 - The reset is nested under the clock IF
 - All logic is in the ELSE

Flip-Flop VHDL

 - Write the VHDL entity and architecture for a D flip-flop with an asynchronous reset



Flip-Flop Variations

- Change the architecture to make the reset synchronous

Flip-Flop Variations



- Change the architecture to add a QN output. Use an internal signal.

Latches

- A basic rule of combinatorial VHDL is :
 - If you assign a value to a signal in the if, you must assign a value to that signal in the elsif (if applicable) and the else
 - Likewise, if you assign a value to a signal in one case, you must assign a value to that signal in all cases
- Why does this rule exist?

What are latches and Why are they bad?

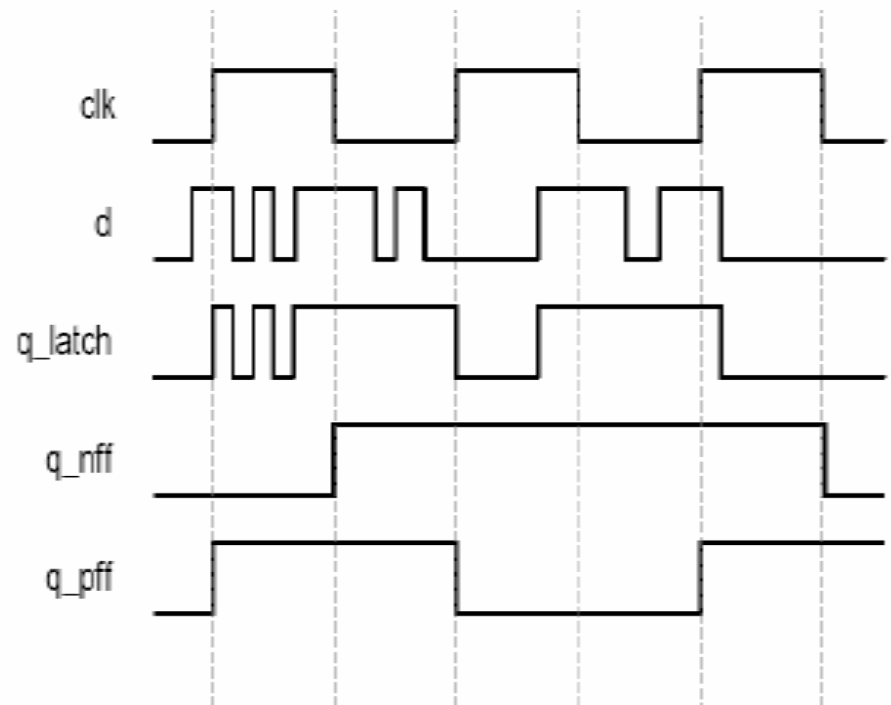 - A latch is level-sensitive – as long as clk is high, q_latch follows d
- The flip-flop is edge-sensitive – q only follows d on the rising or falling edge of clk



Latches (con't)

- To synthesize a D flip flop, use a clocked process


```
dff : process(clk)
begin
    if (clk'event) and (clk='1') then
        q<= d;
    end if;
end process;
```

- Each logic element in the FPGA has a flip-flop built into the hardware
- All of the flip flops in the FPGA are optimized and clocked by a global clock signal
- Properly coded flip flops are implemented in the hardware

Latches (con't)

Figure 2-2 shows a Cyclone II LE.

Figure 2-2. Cyclone II LE

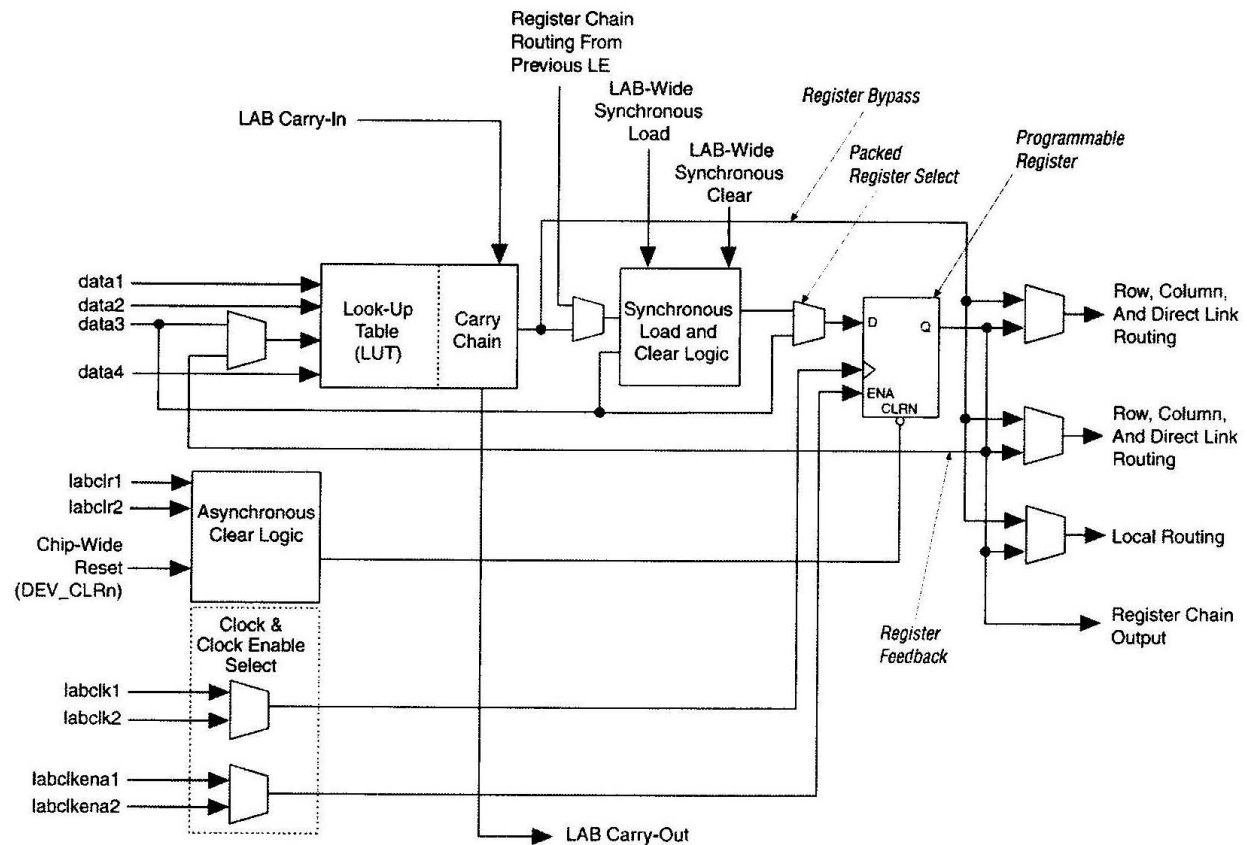

Latches (con't)

- Latches are inferred when a signal is incompletely specified in an if-then-else statement or a case statement.
- The value of the signal is specified in one case but not in the other.
- In the case that the signal is not specified, the signal must maintain its value –
INFERRING MEMORY
- The problem is there is no clock to properly clock the memory

Latches (con't)

- There are no latch elements in the FPGA
- Inferred latches are implemented in the general FPGA gate logic.
- A feedback loop is created
- The static timing analysis will fail as the tools cannot analyze the feedback path.
 - Warning will be generated

Latches (con't)

- Latch Example

Latch : process (c, d)

begin



if (c = '1') then

q_latch <= d;

end if;

End process;

q <= q_latch;

  

Latches - Final

- Latches are bad and should be avoided
 - The synthesizer will warn you if you have inferred a latch
 - Do not ignore the warning.
 - Simple designs may still work, but more complex designs have been seen to fail